



CPE 221: Computer Organization

15 Multicycle ARM Processor
rahul.bhadani@uah.edu

Rahul Bhadani

Multicycle ARM Processor

- **Single-cycle:**
 - + simple
 - cycle time limited by longest instruction (LDR)
 - separate memories for instruction and data
 - 3 adders/ALUs – ADDERS are expensive circuits
- **Multicycle processor addresses these issues by breaking instruction into shorter steps**
 - a. shorter instructions take fewer steps
 - b. can re-use hardware
 - c. cycle time is faster
 - d. read/write the memory/register or use the ALU
 - e. instruction read in one step, data written in a later step – thus need only single memory for instruction and data.

Multicycle ARM Processor

- **Multicycle:**

- + higher clock speed
- + simpler instructions run faster
- + reuse expensive hardware on multiple cycles
- sequencing overhead paid many times

Same design steps as single-cycle:


- first datapath
- then control

In addition:

- circuitry to store the intermediate results


Multicycle State Elements

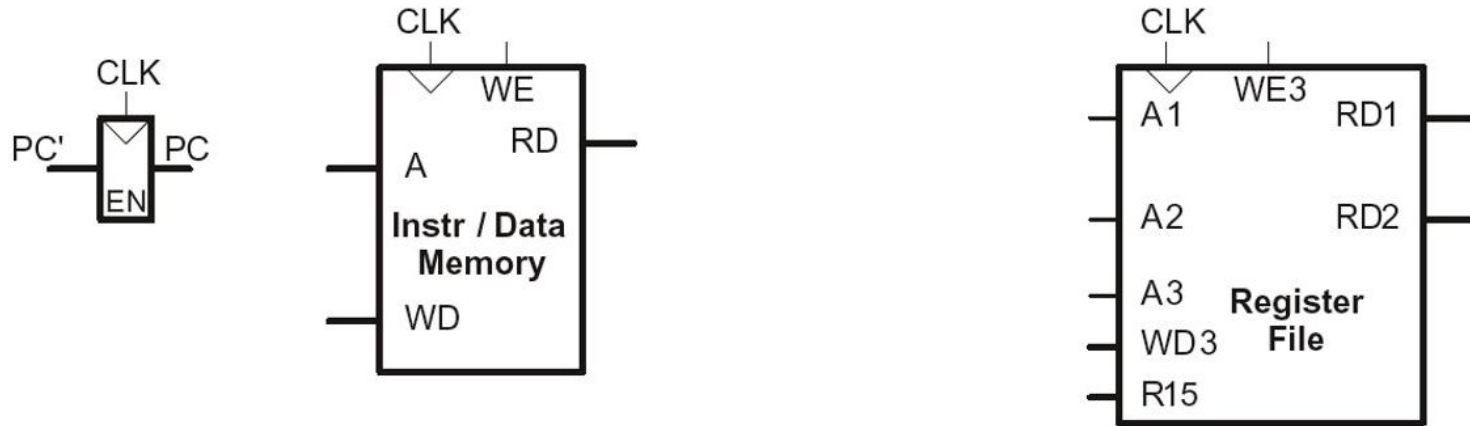Replace Instruction and Data memories with a single unified memory – more realistic




Instruction Register

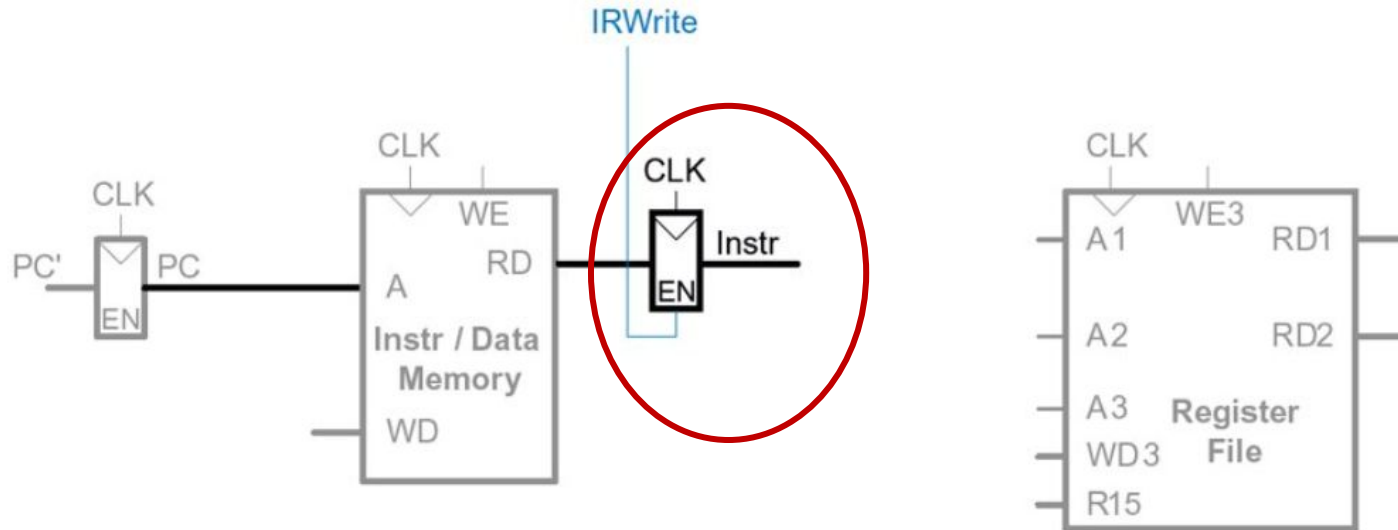The instruction is read and stored in a new non-architectural instruction register (IR) so that it is available for future cycles. The IR receives an enable signal, called IRWrite, which is asserted when the IR should be loaded with a new instruction.




Multicycle Datapath: Instruction Fetch

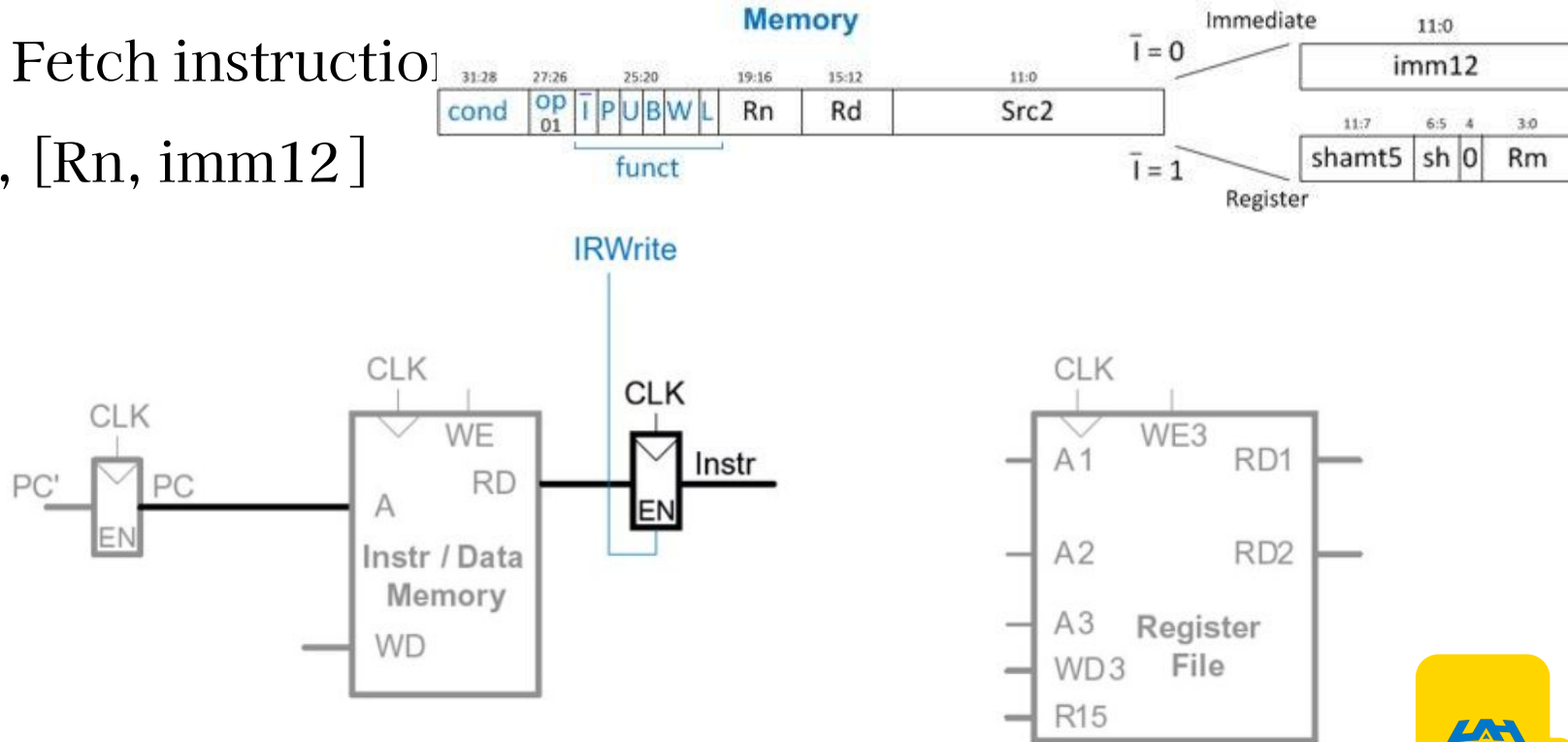STEP 1: Fetch instruction
LDR Rd, [Rn, imm12]



Multicycle Datapath: LDR Register Read


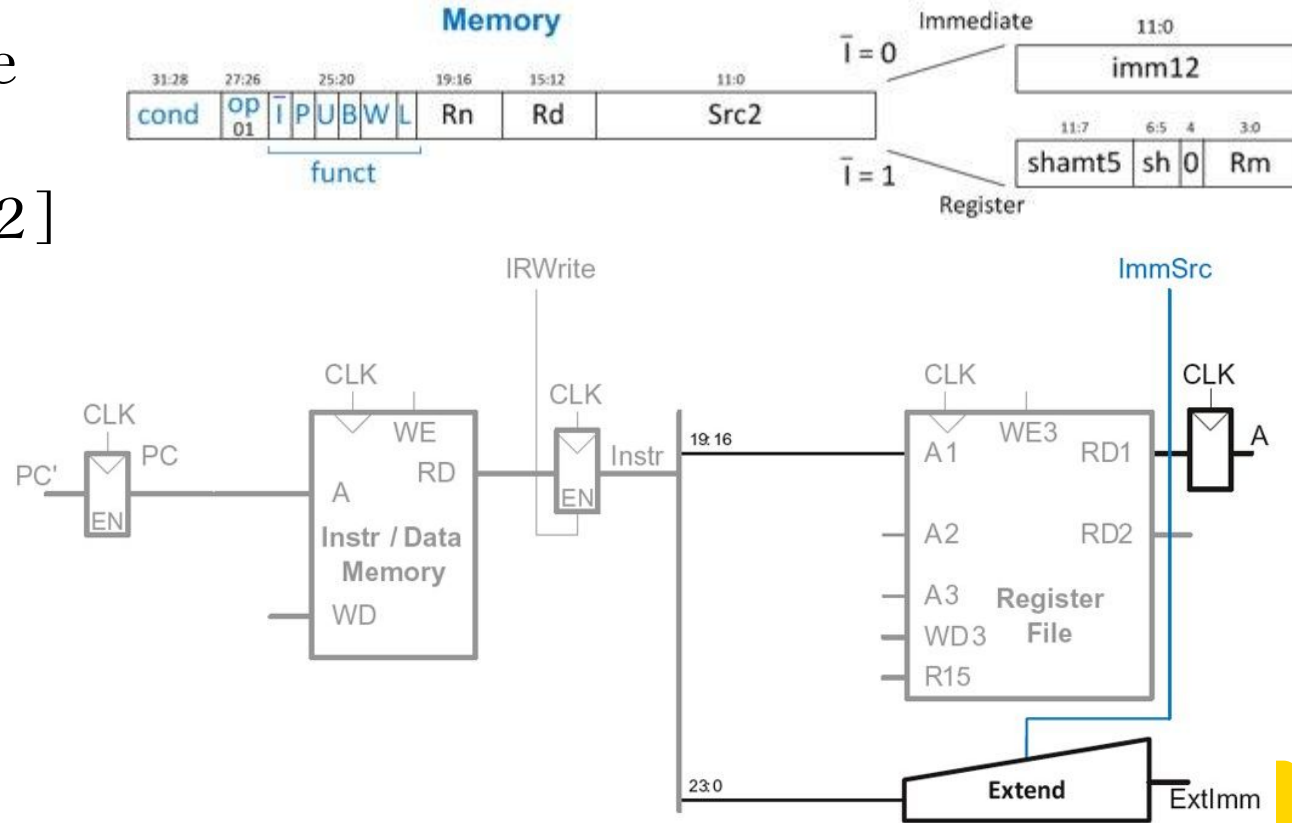
STEP 2: Read source operands from RF
LDR Rd, [Rn, imm12]



Multicycle Datapath: LDR Address



STEP 3: Compute the memory address

LDR Rd, [Rn, imm12]

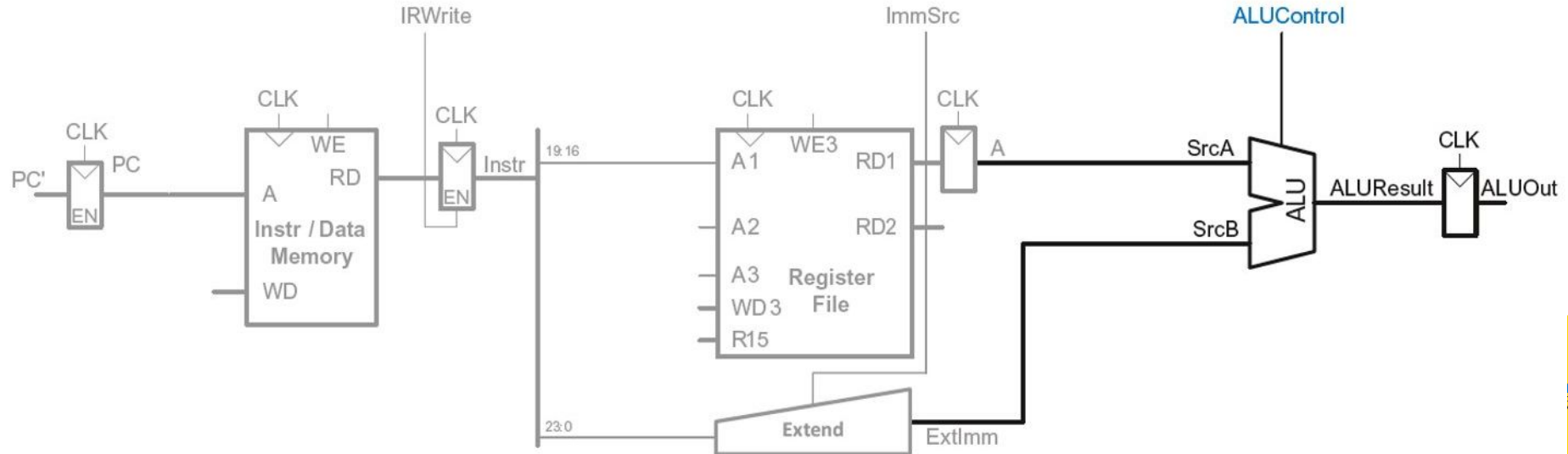 



Multicycle Datapath: LDR Memory Read

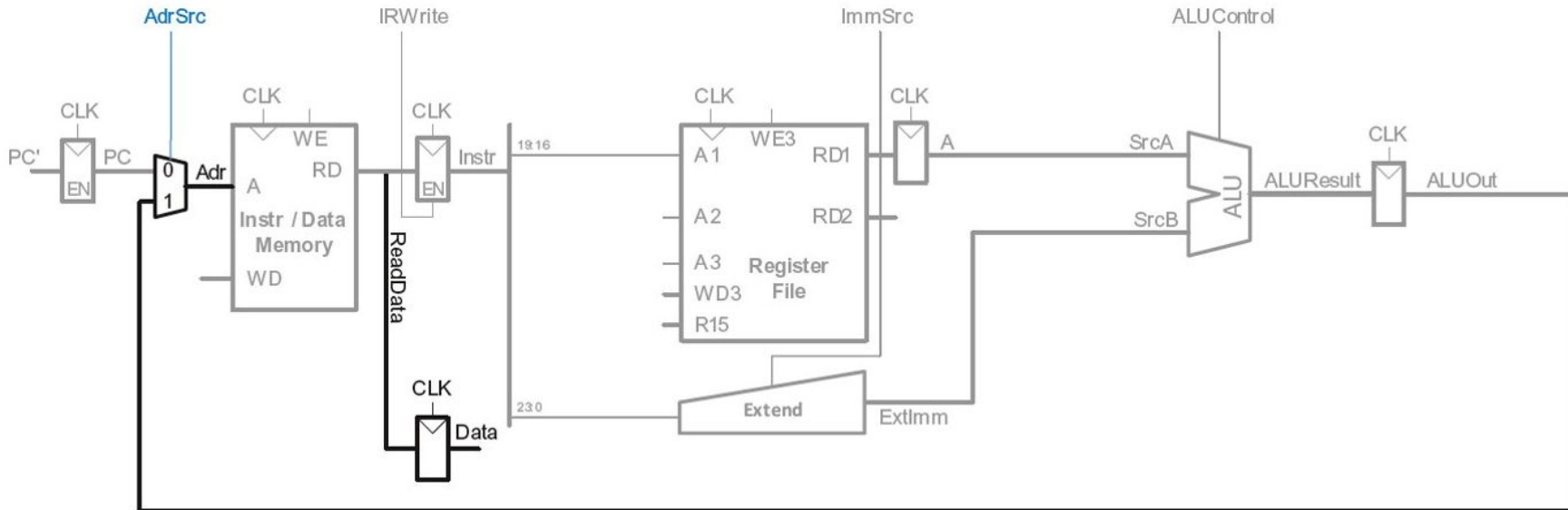 STEP 4: Read data from memory
LDR Rd, [Rn, imm12]




Multicycle Datapath: LDR Write Register

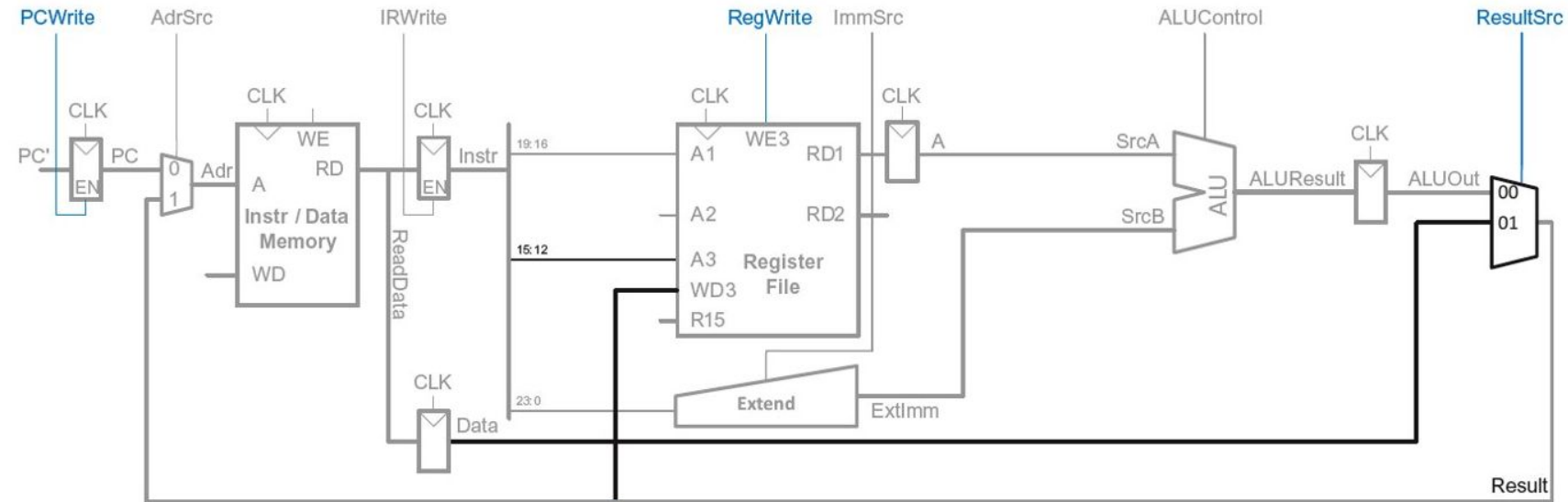 STEP 5: Write data back
to register file
LDR Rd, [Rn, imm12]




Multicycle Datapath: Increment PC

STEP 6: Increment PC

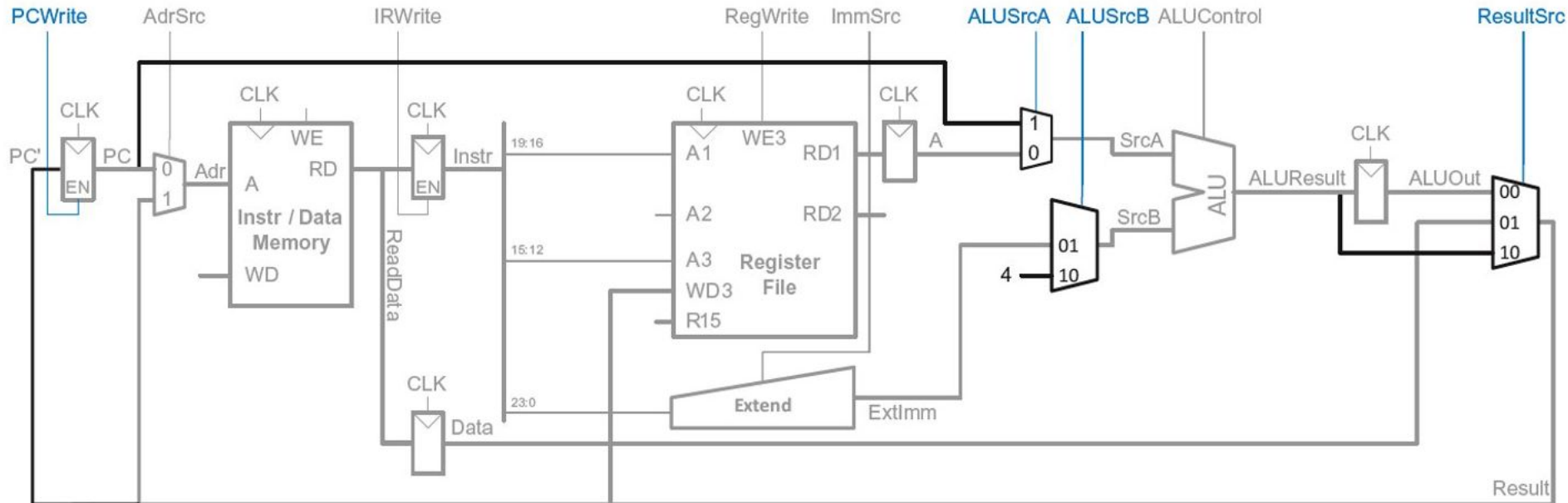

Multicycle Datapath: Access to PC


PC can be read/written by instruction

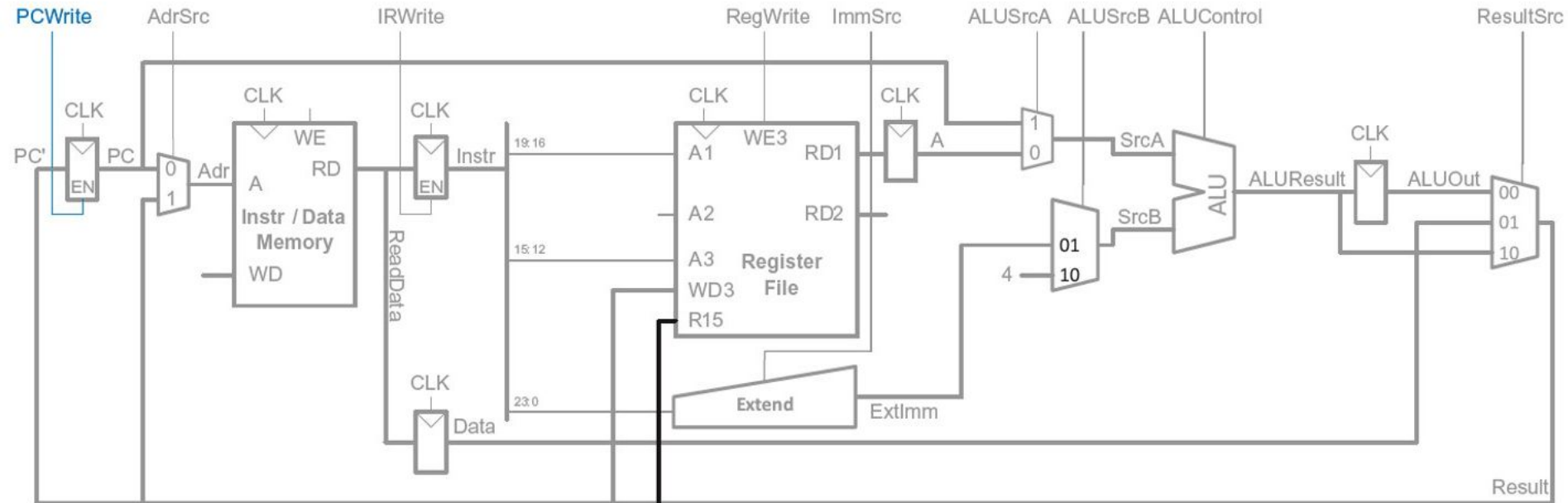

Multicycle Datapath: Access to PC

PC can be read/written by instruction

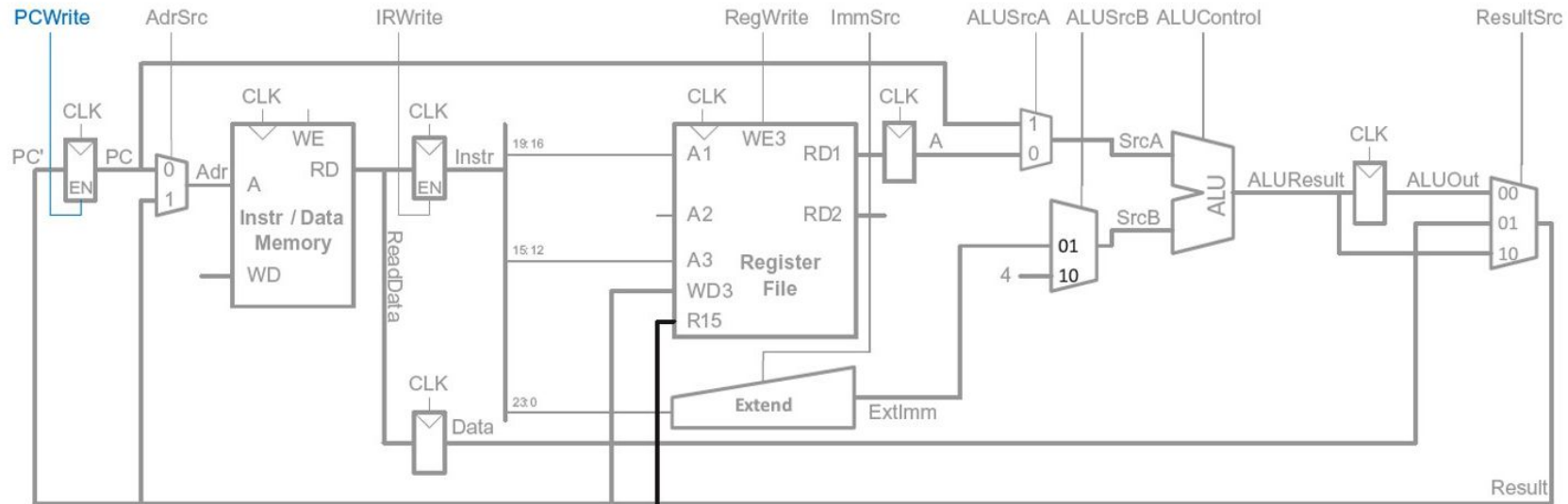
- **Read:** R15 (PC+8) available in Register File



Multicycle Datapath: Read to PC (R15)

Example: ADD R1, R15, R2

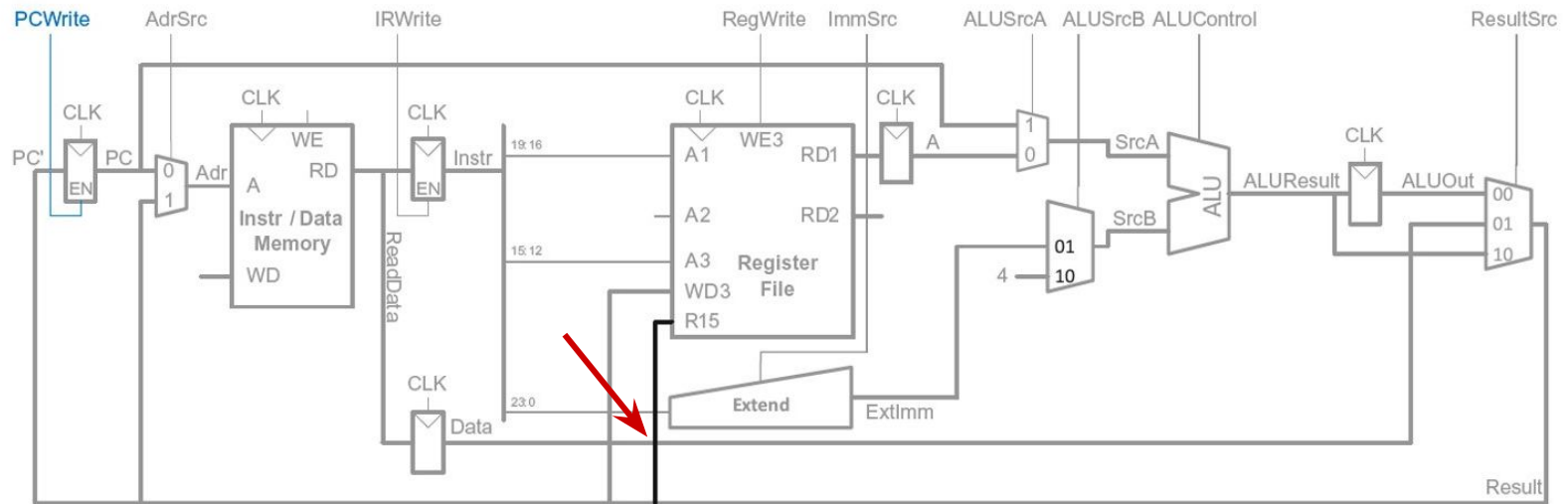
1. R15 needs to be read as PC+8 from Register File (RF) in 2nd step
2. So (also in 2nd step) PC + 8 is produced by ALU and routed to R15 input of RF



Multicycle Datapath: Access to PC

PC can be read/written by instruction

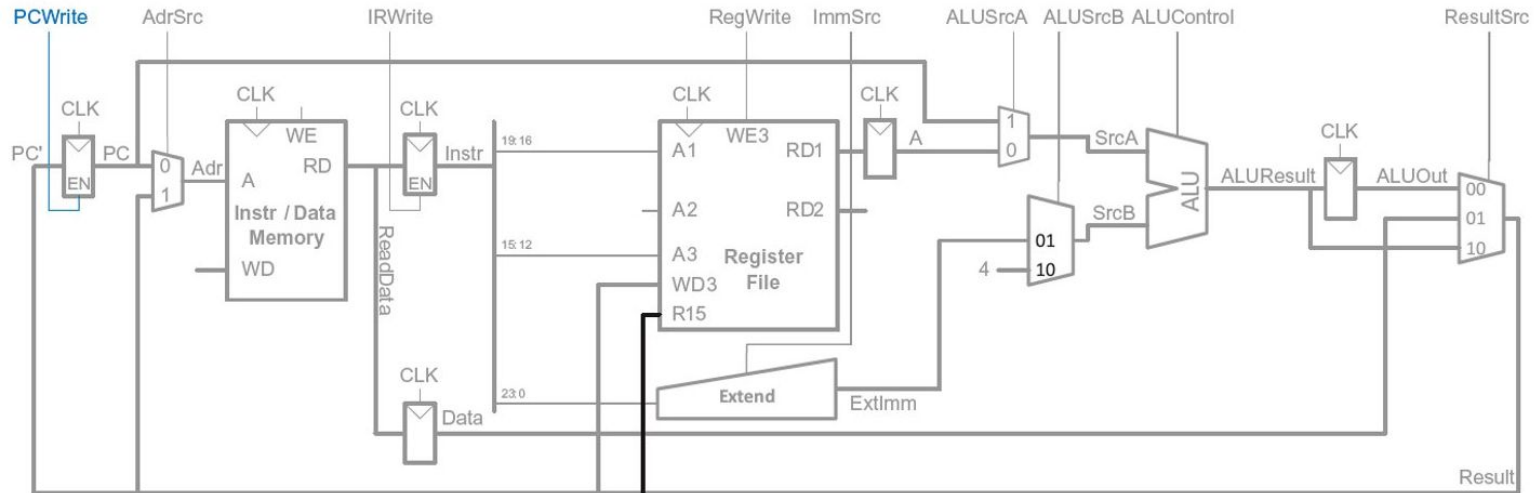
- **Read:** R15 (PC+8) available in Register File
- **Write:** Be able to write result of instruction to PC



Multicycle Datapath: Write to PC (R15)


Example: SUB R15, R8, R3

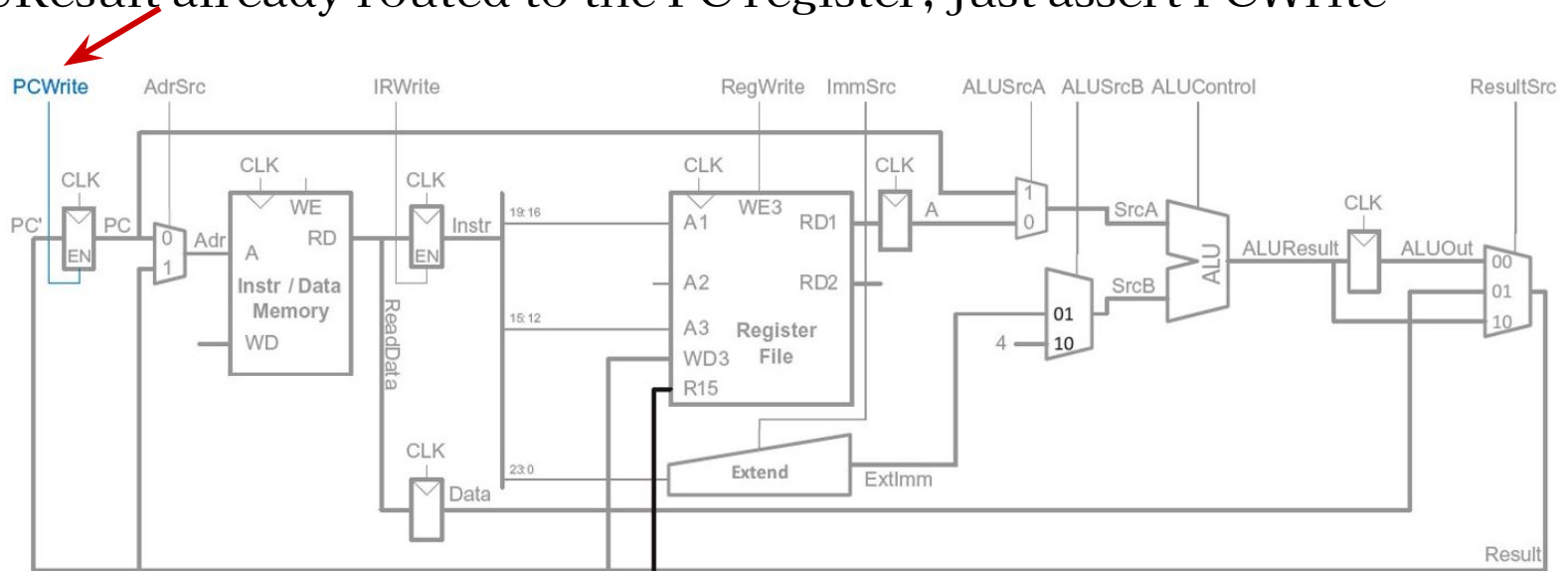1. Result of instruction needs to be written to the PC register
2. ALUResult already routed to the PC register, just assert PCWrite




Multicycle Datapath: STR

Write data in Rn to memory

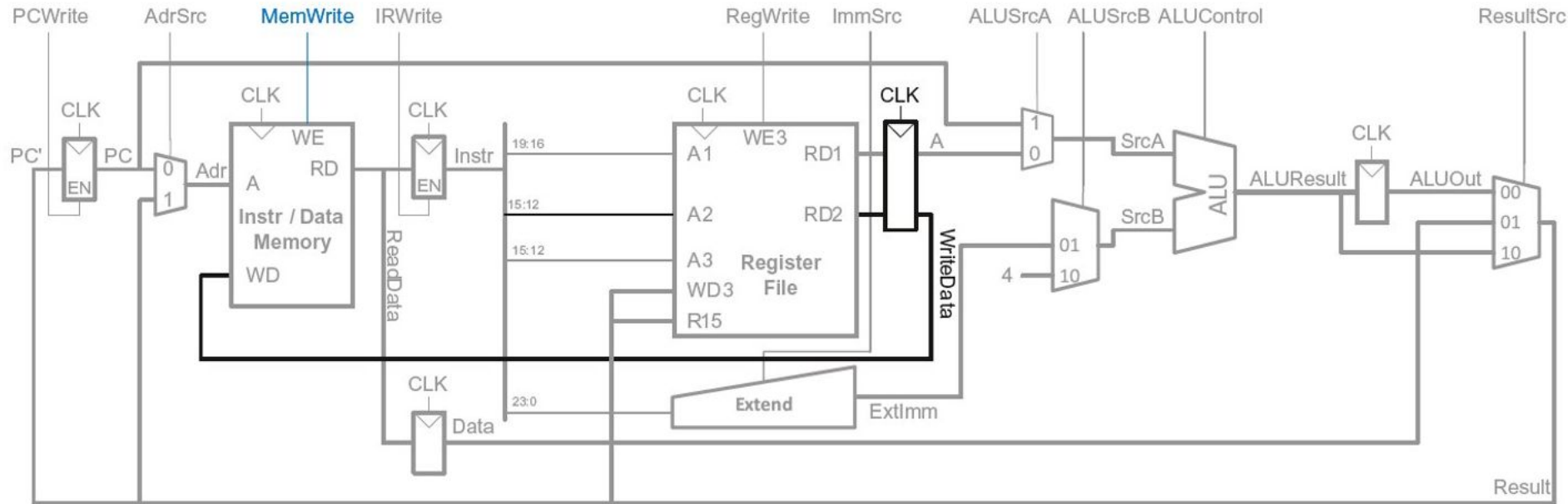


Multicycle Datapath: Data-processing

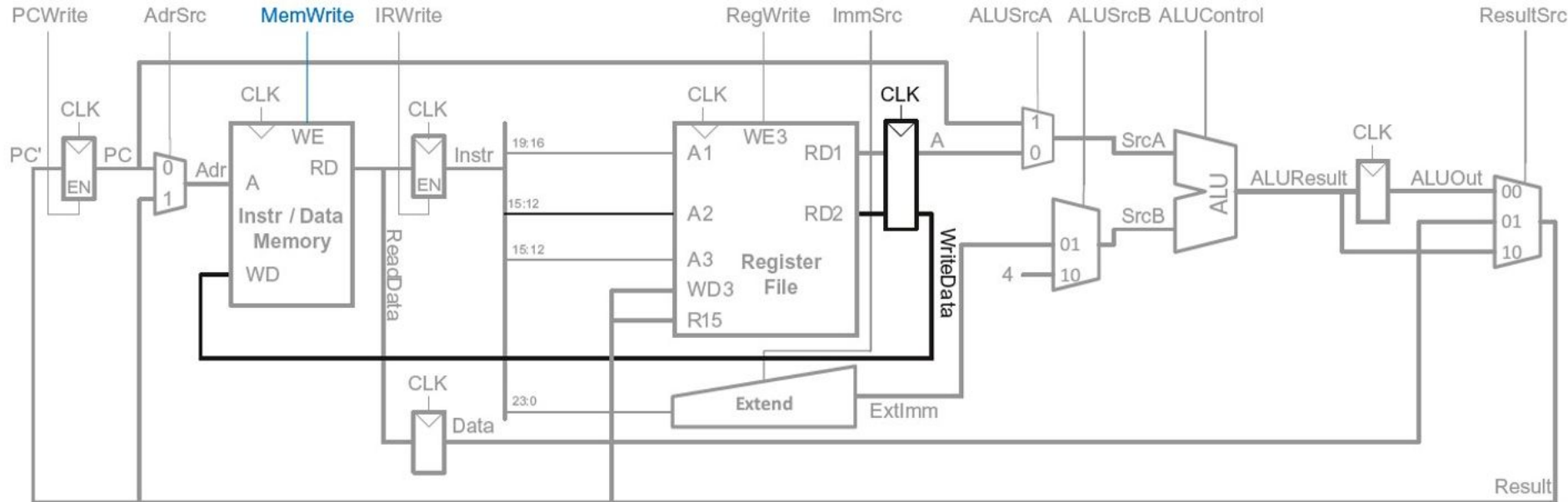With immediate addressing (i.e., an immediate *Src2*), no additional changes needed for datapath



Multicycle Datapath: Data-processing

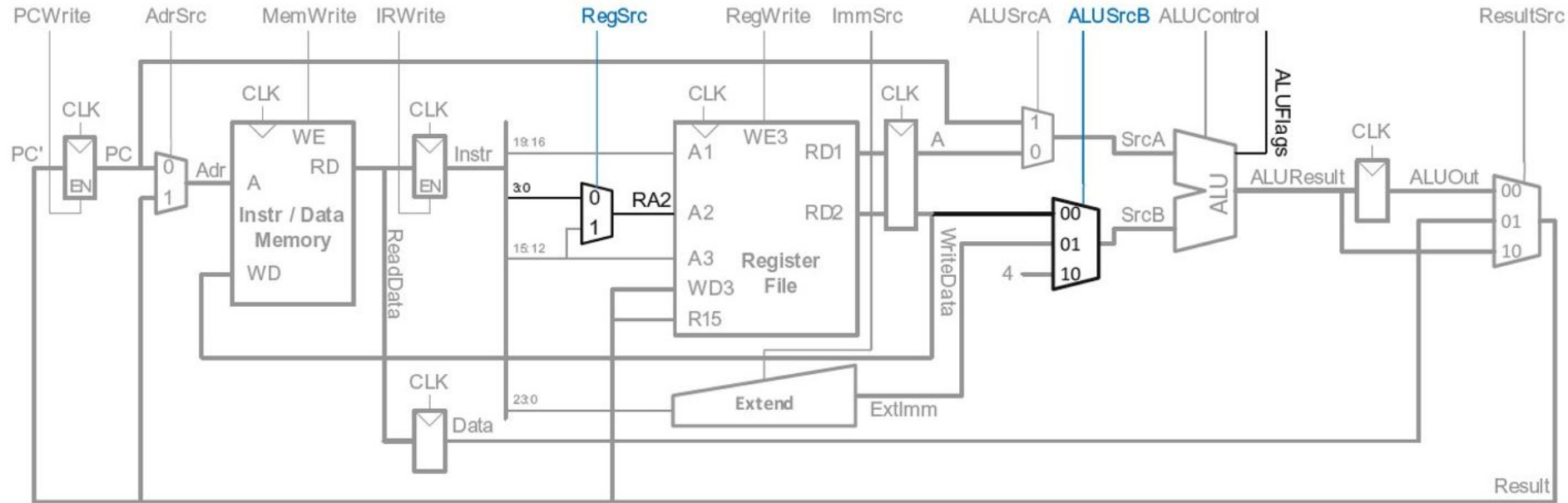With register addressing (register *Src2*):
Read from Rn and Rm




Multicycle Datapath: B


Calculate branch target address:

$$BTA = (ExtImm) + (PC+8)$$
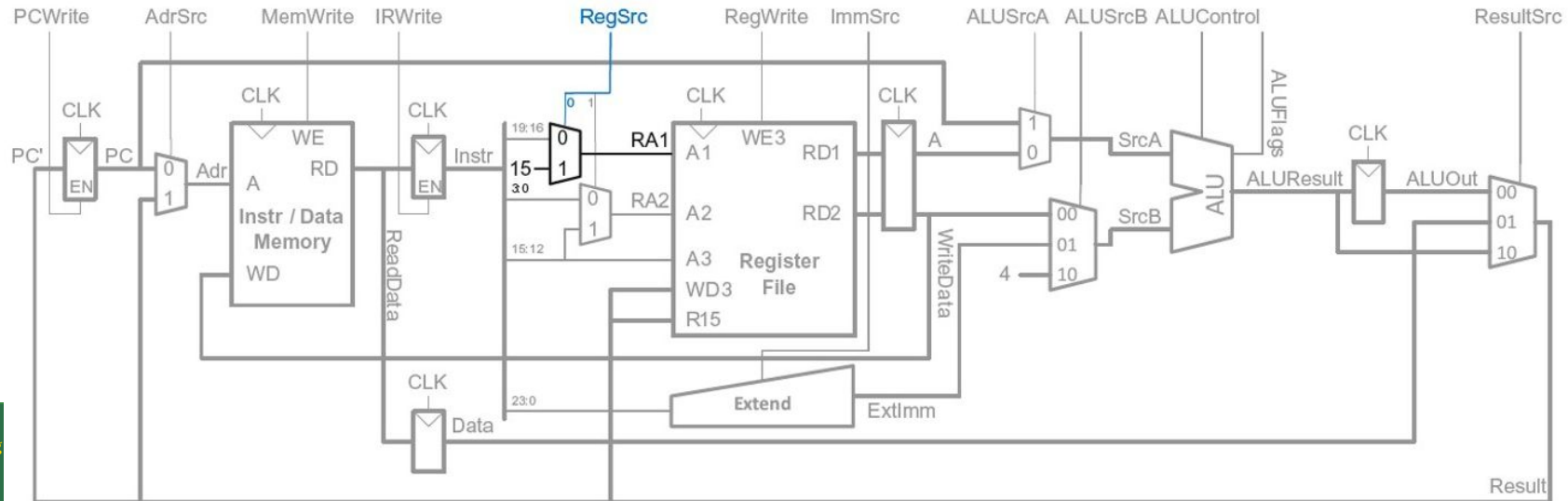
$$ExtImm = Imm24 \ll 2 \text{ and sign-extended}$$




Multicycle ARM Processor (Control Unit)

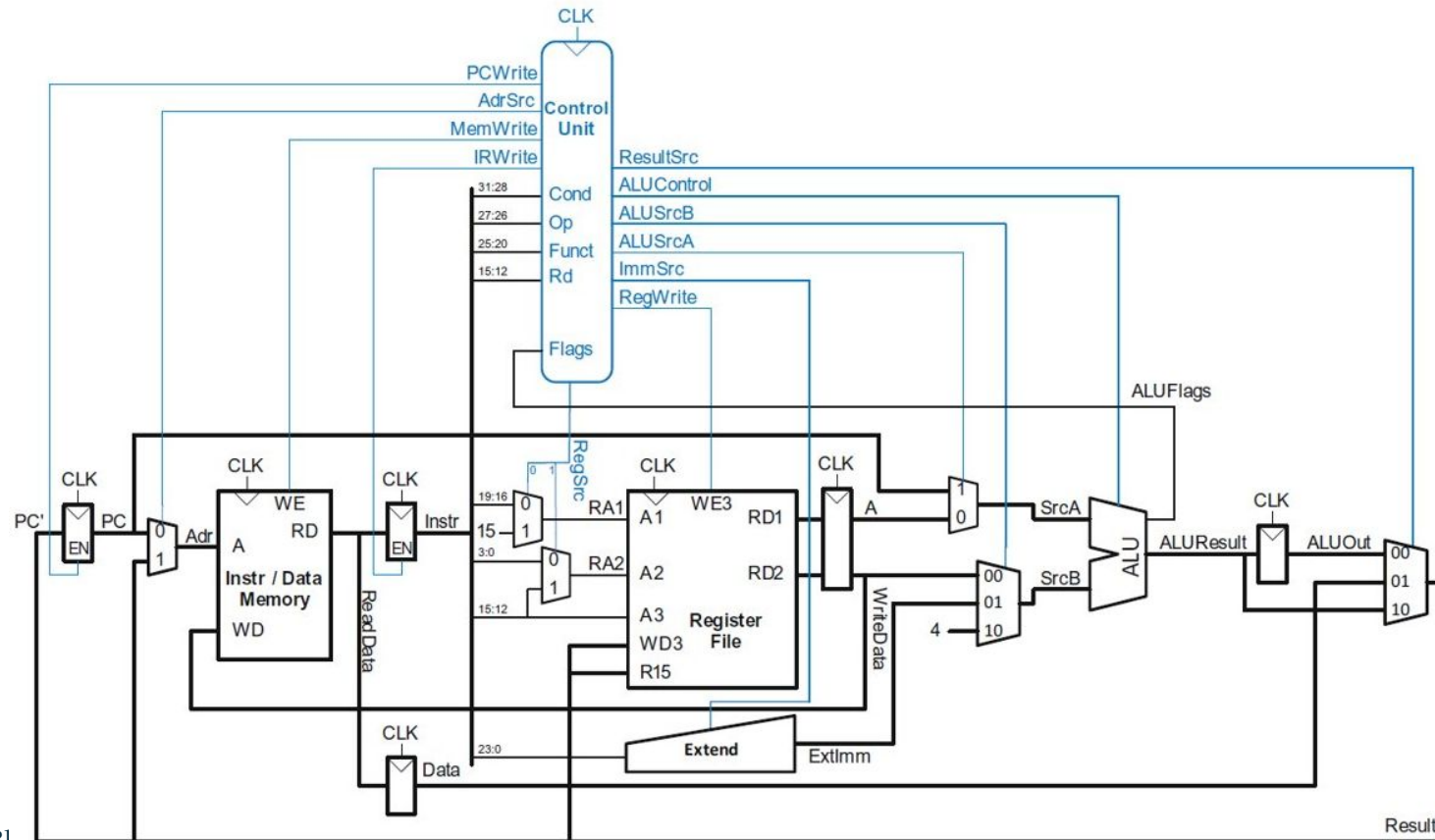


Multicycle Control

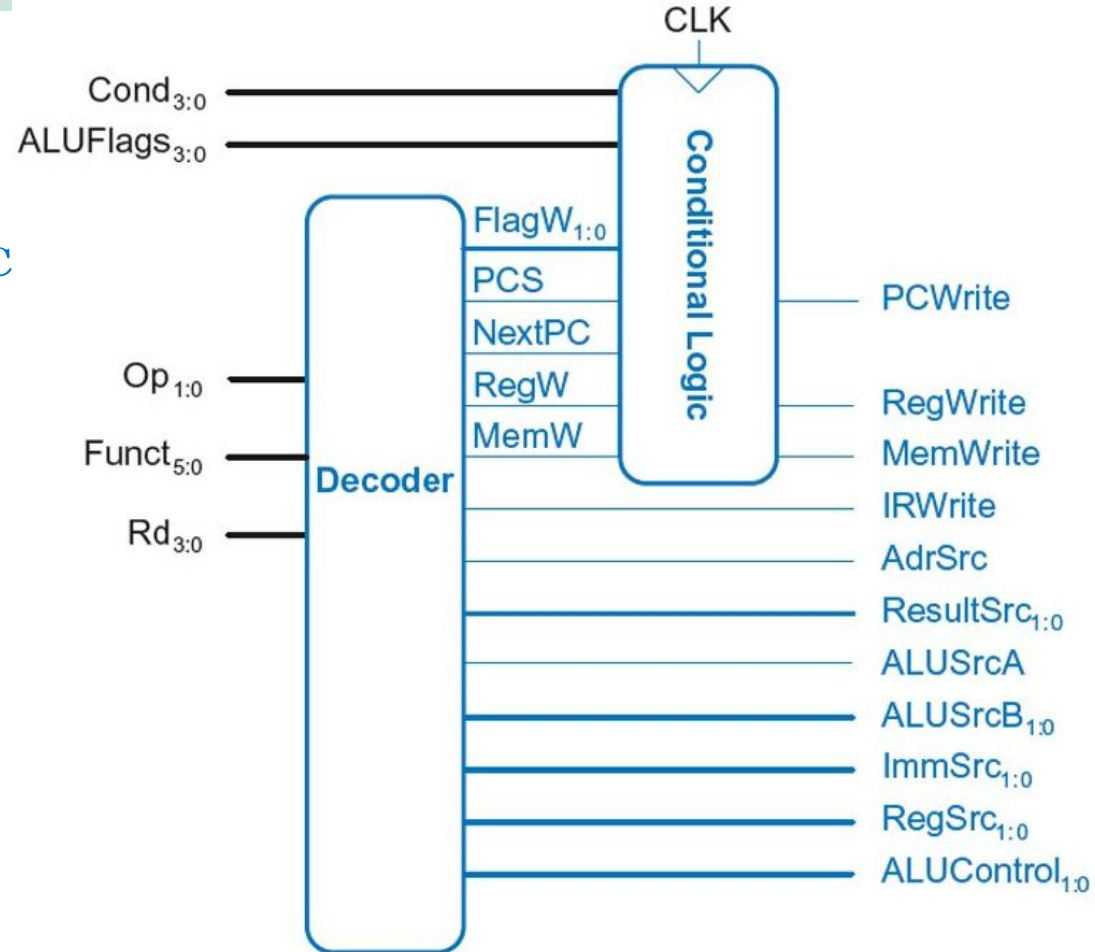- First, discuss **Decoder**
- Then, **Conditional Logic**




Multicycle Control: Decoder

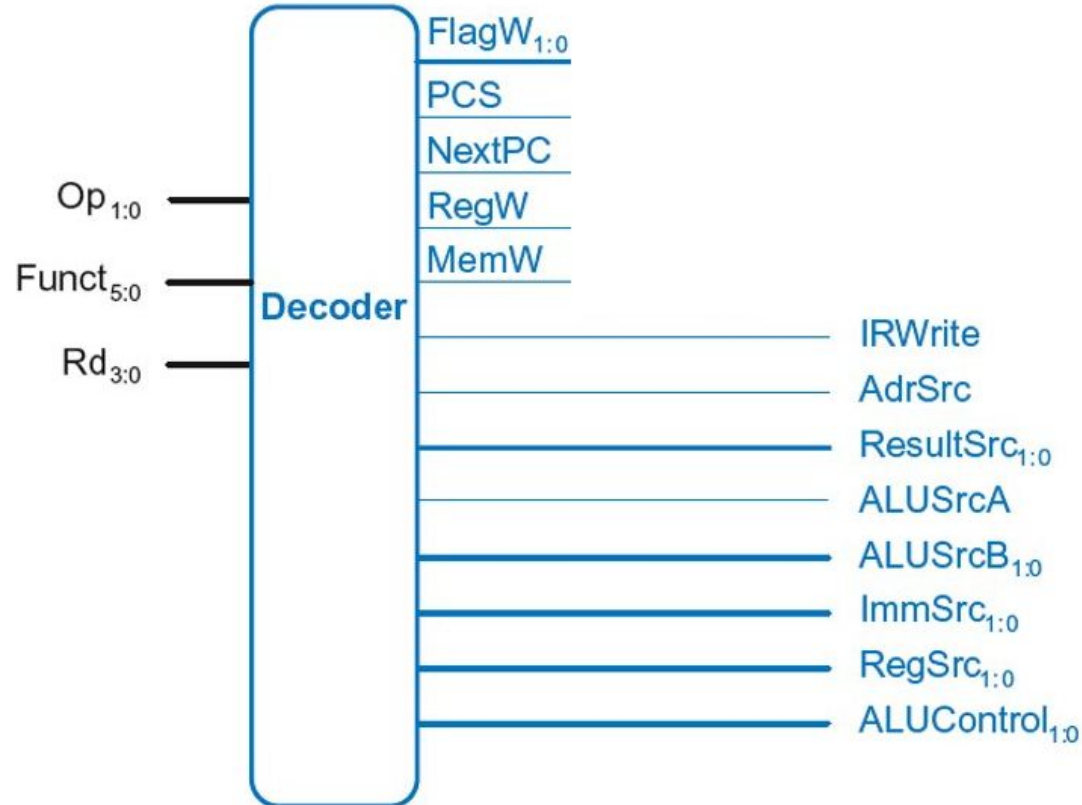

Multicycle Control: Unwrapping Decoder

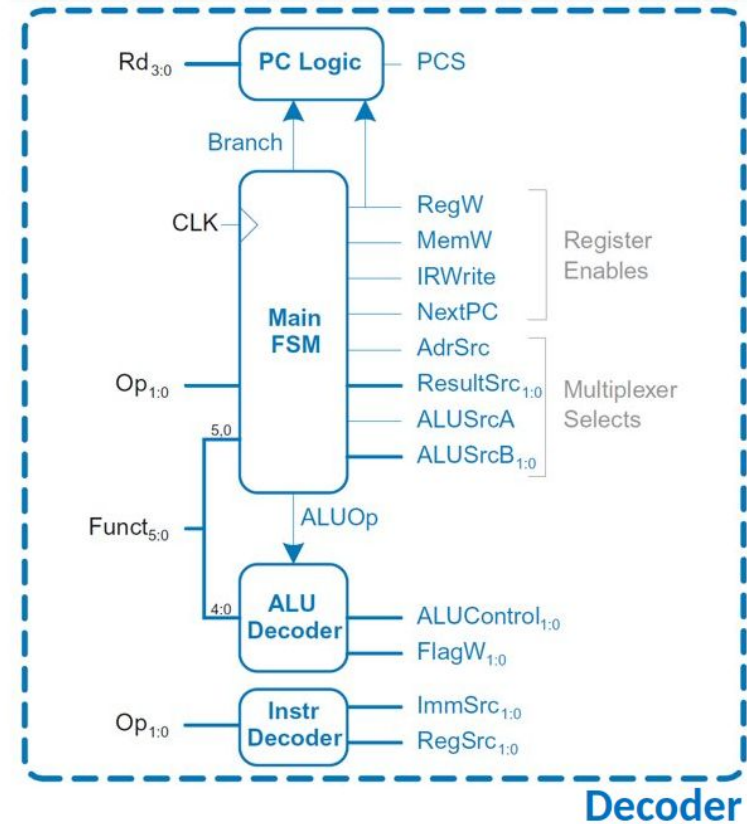ALU Decoder and PC Logic
same as single-cycle




Multicycle Control: Instr Decoder

$RegSrc_0 = (Op == 10_2)$


$RegSrc_1 = (Op == 01_2)$

$ImmSrc_{1:0} = Op$

 


Instruction	Op	Funct ₅	Funct ₀	RegSrc ₀	RegSrc ₁	ImmSrc _{1:0}
LDR	01	X	1	0	X	01
STR	01	X	0	0	1	01
DP immediate	00	1	X	0	X	00
DP register	00	0	X	0	0	00
B	10	X	X	1	X	10


Multicycle Control: Main FSM

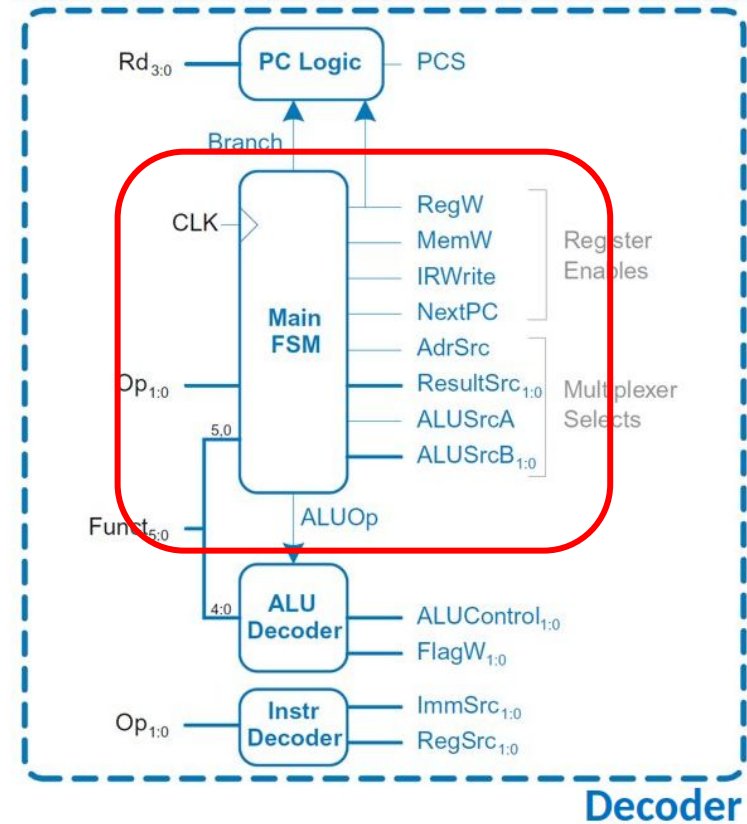



Main Controller FSM: Fetch

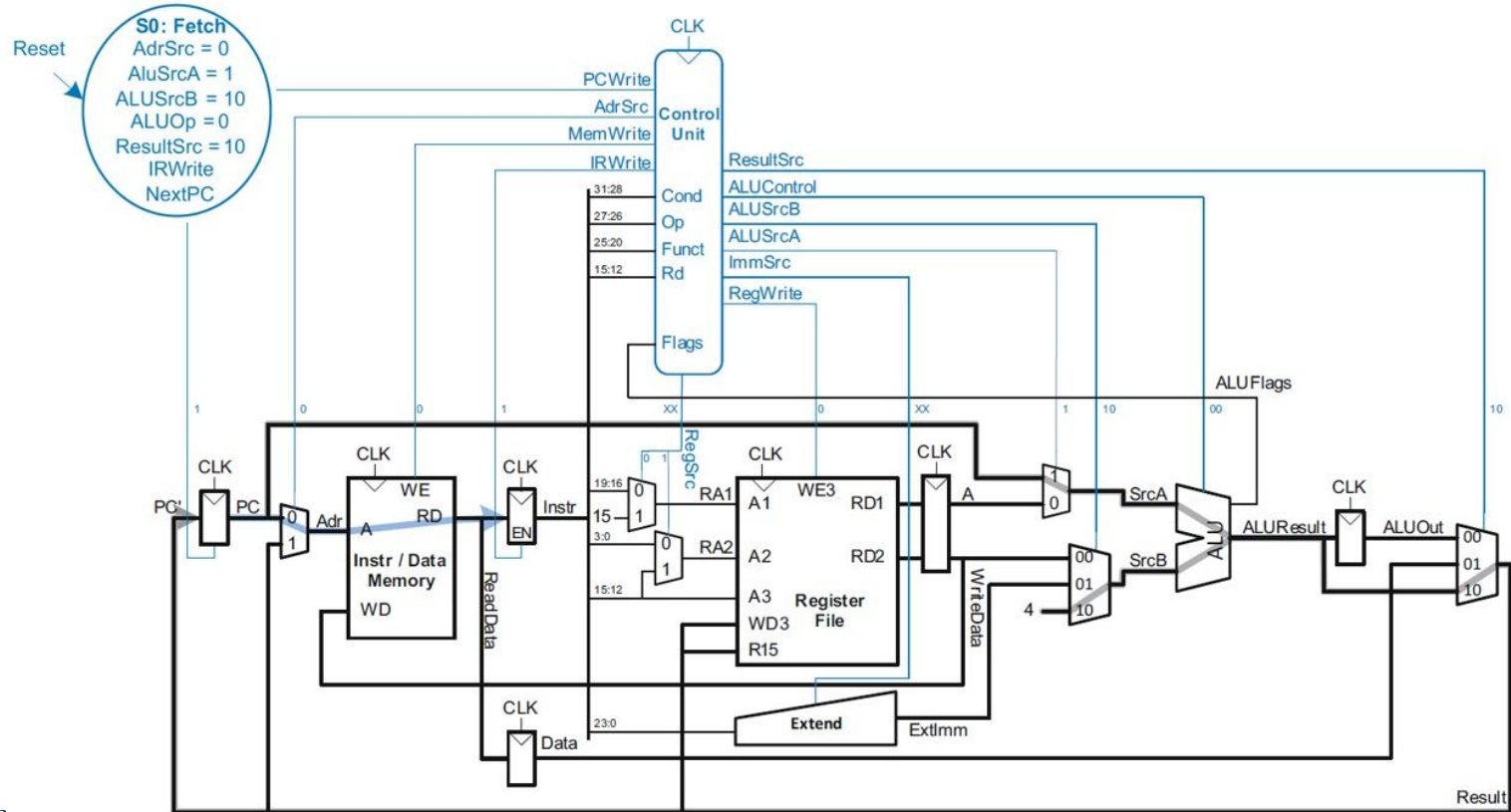


Main Controller FSM: Decode

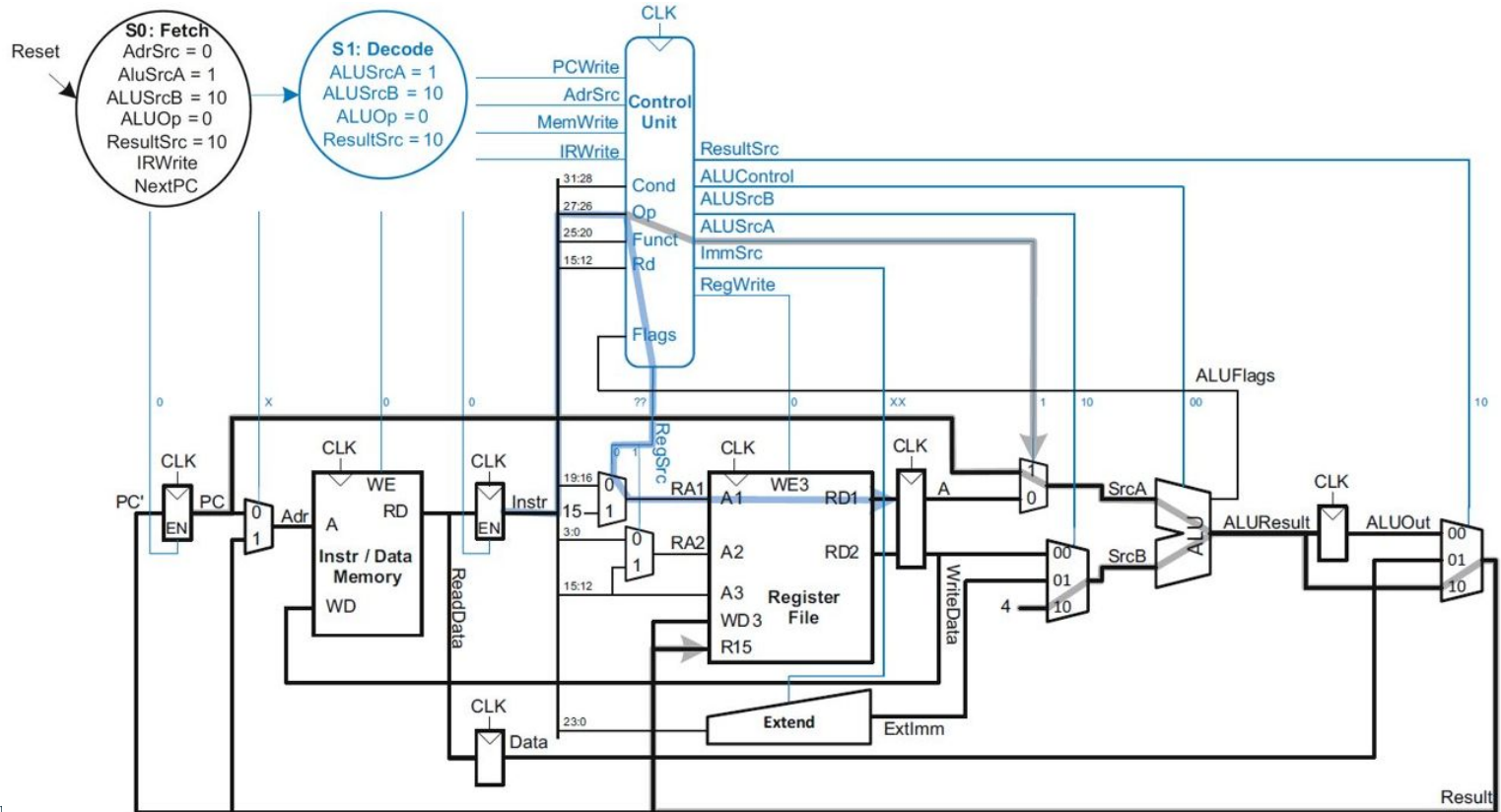


Main Controller FSM: Address

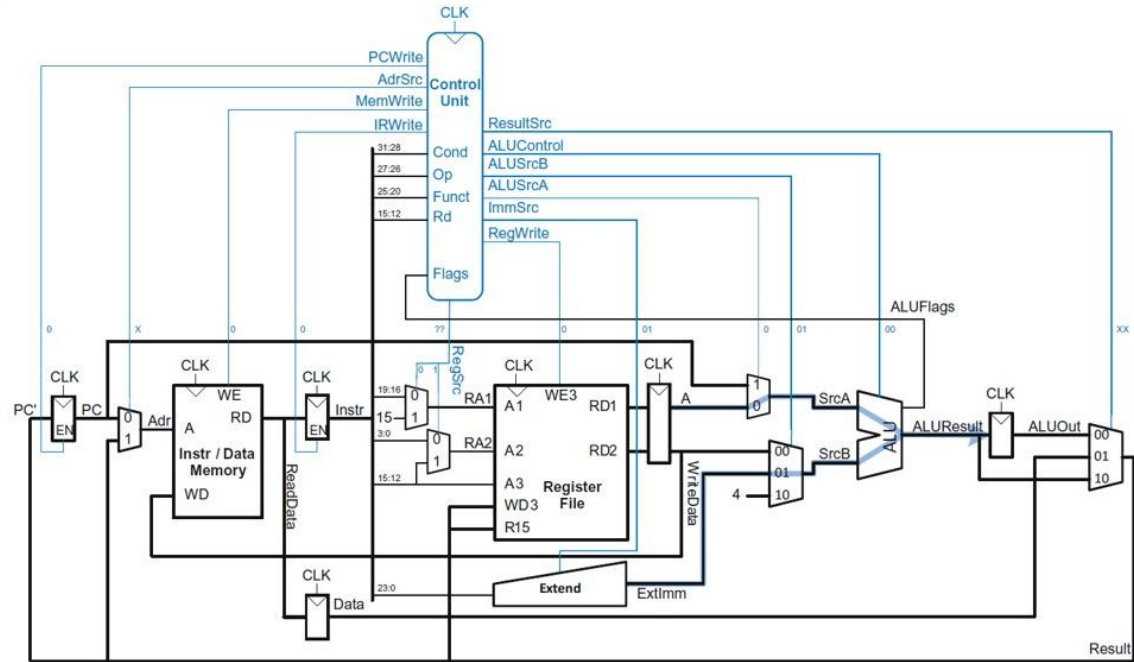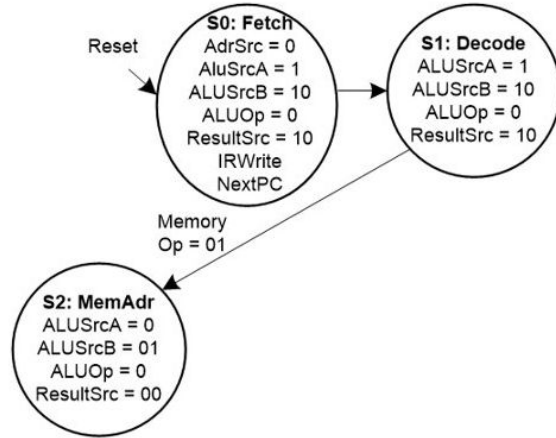


Main Controller FSM: Read Memory

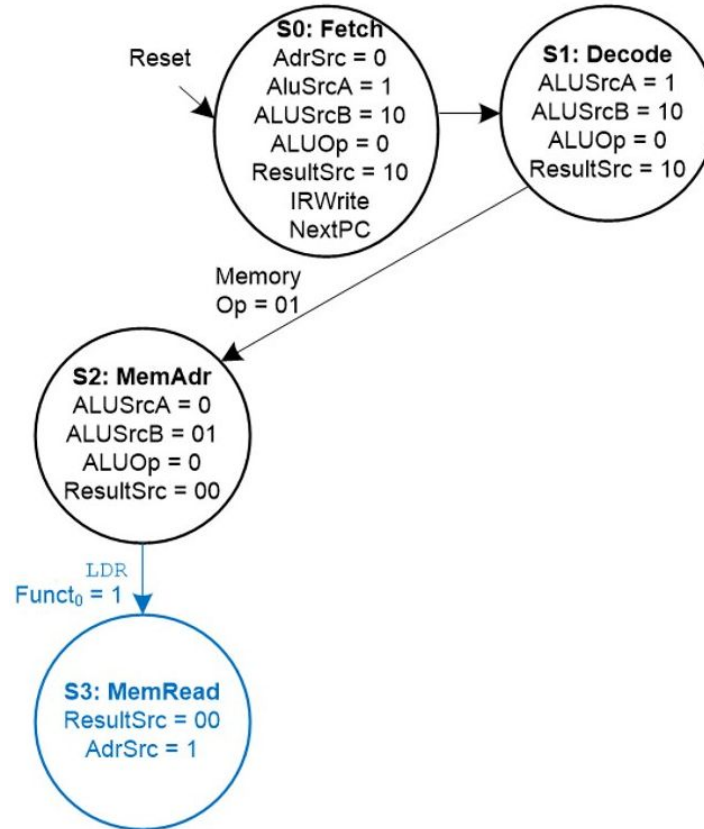


Main Controller FSM: LDR

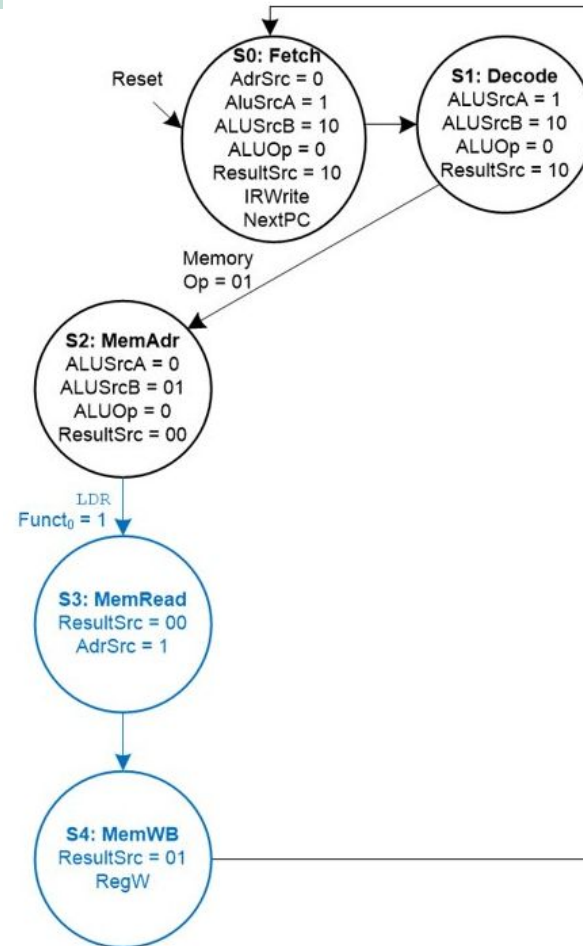

Main Controller FSM: STR

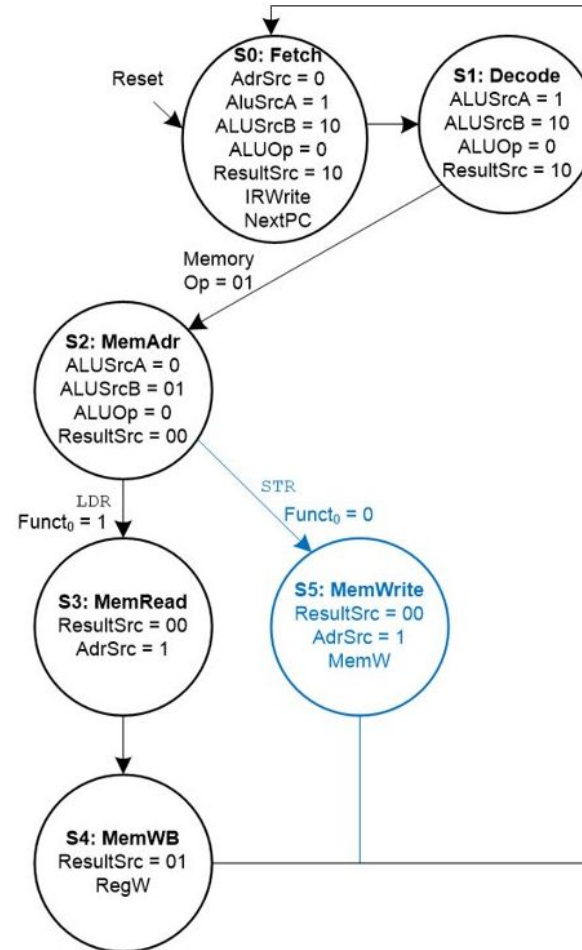

Main Controller FSM: Data-processing

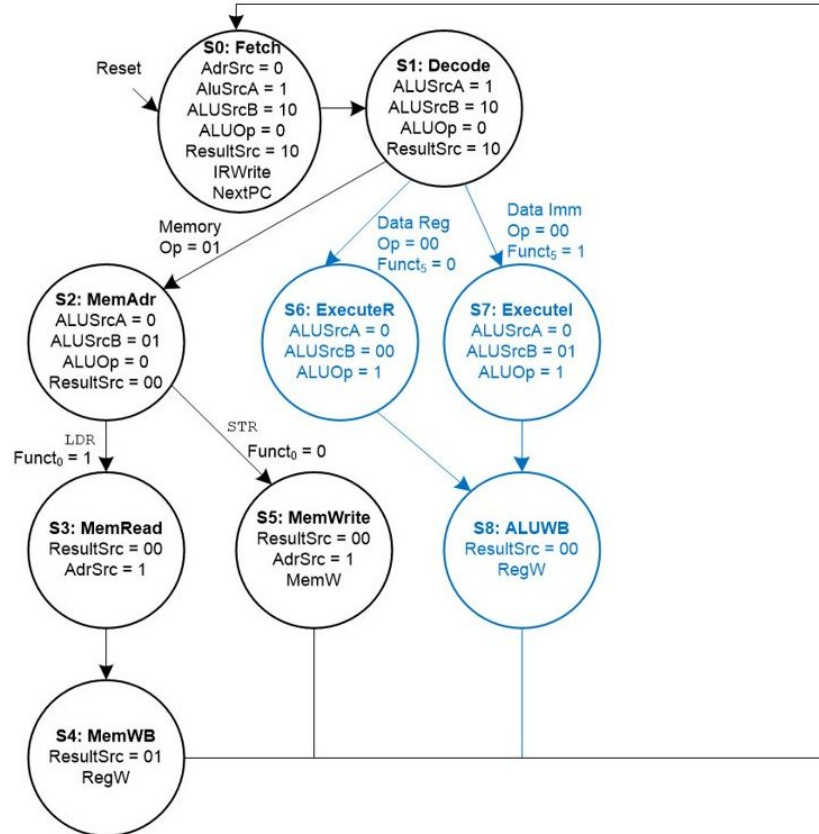

Multicycle Controller FSM

State

Fetch

Decode

MemAdr

MemRead

MemWB

MemWrite

ExecuteR

ExecuteI

ALUWB

Branch

Datapath μ Op

Instr \leftarrow Mem[PC]; PC \leftarrow PC+4

ALUOut \leftarrow PC+4

ALUOut \leftarrow Rn + Imm

Data \leftarrow Mem[ALUOut]

Rd \leftarrow Data


Mem[ALUOut] \leftarrow Rd

ALUOut \leftarrow Rn op Rm


ALUOut \leftarrow Rn op Imm

Rd \leftarrow ALUOut


PC \leftarrow R15 + offset

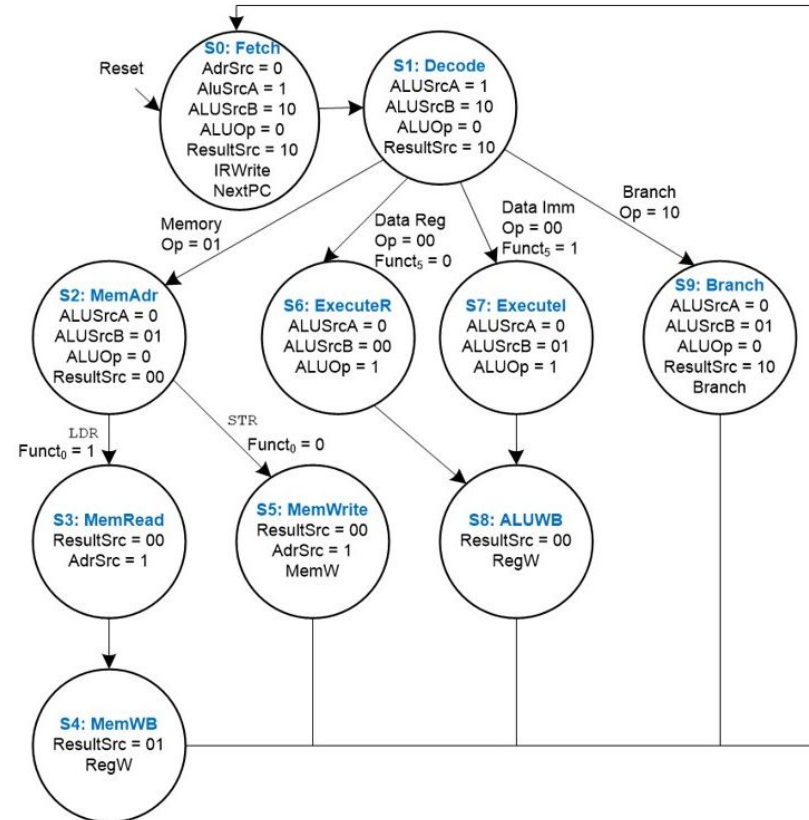


Multicycle Control: Cond. Logic

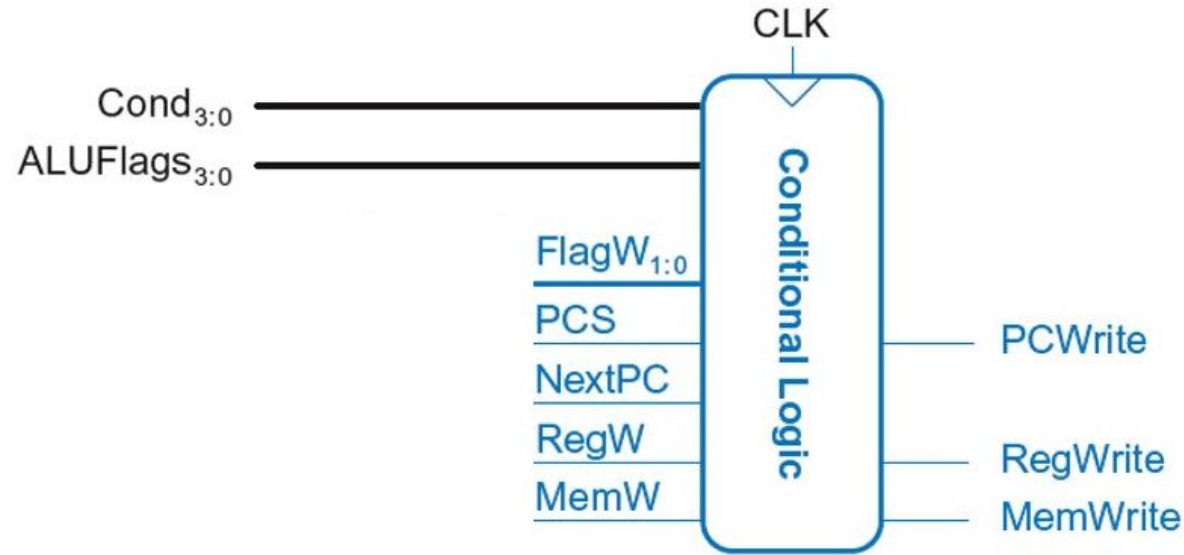

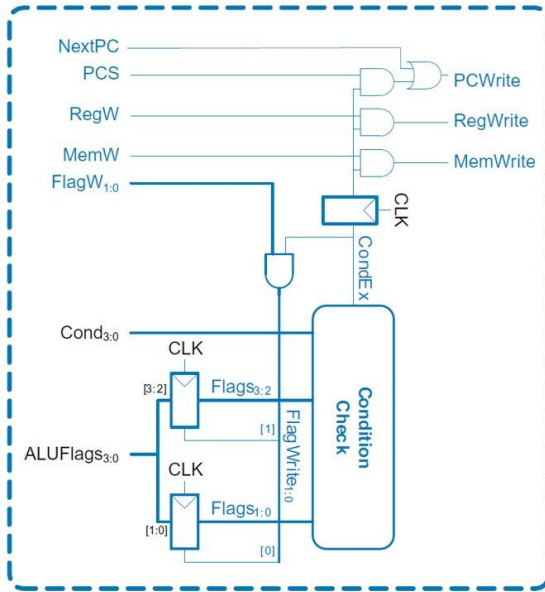Single-Cycle vs Multi-cycle Conditional Logic



Single-Cycle

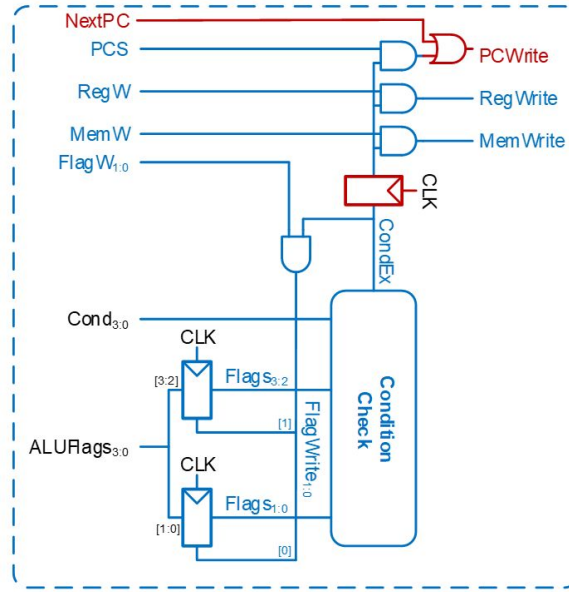

Multi-Cycle

- PCWrite asserted in Fetch state
- ExecuteI/ExecuteR state:
CondEx asserts
ALUFlags generated
- ALUWB state:
Flags updated
CondEx changes
PCWrite, *RegWrite*, and *MemWrite* don't see change till new instruction (Fetch state)

Multicycle Processor Performance

- Instructions take different number of cycles:
 - 3 cycles: B
 - 4 cycles: DP, STR
 - 5 cycles: LDR
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type

<https://www.spec.org/cpu2000/CINT2000/>

$$\text{Average CPI} = (0.13)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$

Multicycle Processor Performance

Multicycle critical path:

- Assumptions:
 - RF is faster than memory
 - writing memory is faster than reading memory

$$T_{c_2} = t_{pcq} + 2t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$

$$T_{c_2} = ?$$

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

Multicycle Processor Performance

Multicycle critical path:

- Assumptions:
 - RF is faster than memory
 - writing memory is faster than reading memory

$$T_{c_2} = t_{pcq} + 2t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$

$$\begin{aligned} T_{c_2} &= t_{pcq} + 2t_{mux} + \max[t_{ALU} + t_{mux}, \\ &\quad t_{mem}] + t_{setup} \\ &= [40 + 2(25) + 200 + 50] \text{ ps} = \\ &\quad 340 \text{ ps} \end{aligned}$$

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** ARM processor

- CPI = 4.12 cycles/instruction
- Clock cycle time: $T_{c2} = 340$ ps

Execution Time = ?

Multicycle Performance Example


For a program with **100 billion** instructions executing on a **multicycle** ARM processor

- CPI = 4.12 cycles/instruction
- Clock cycle time: $T_{c2} = 340$ ps


$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(340 \times 10^{-12}) \\ &= 140 \text{ seconds}\end{aligned}$$

This is **slower** than the single-cycle processor (84 sec.)


Recap Single-Cycle ARM Processor

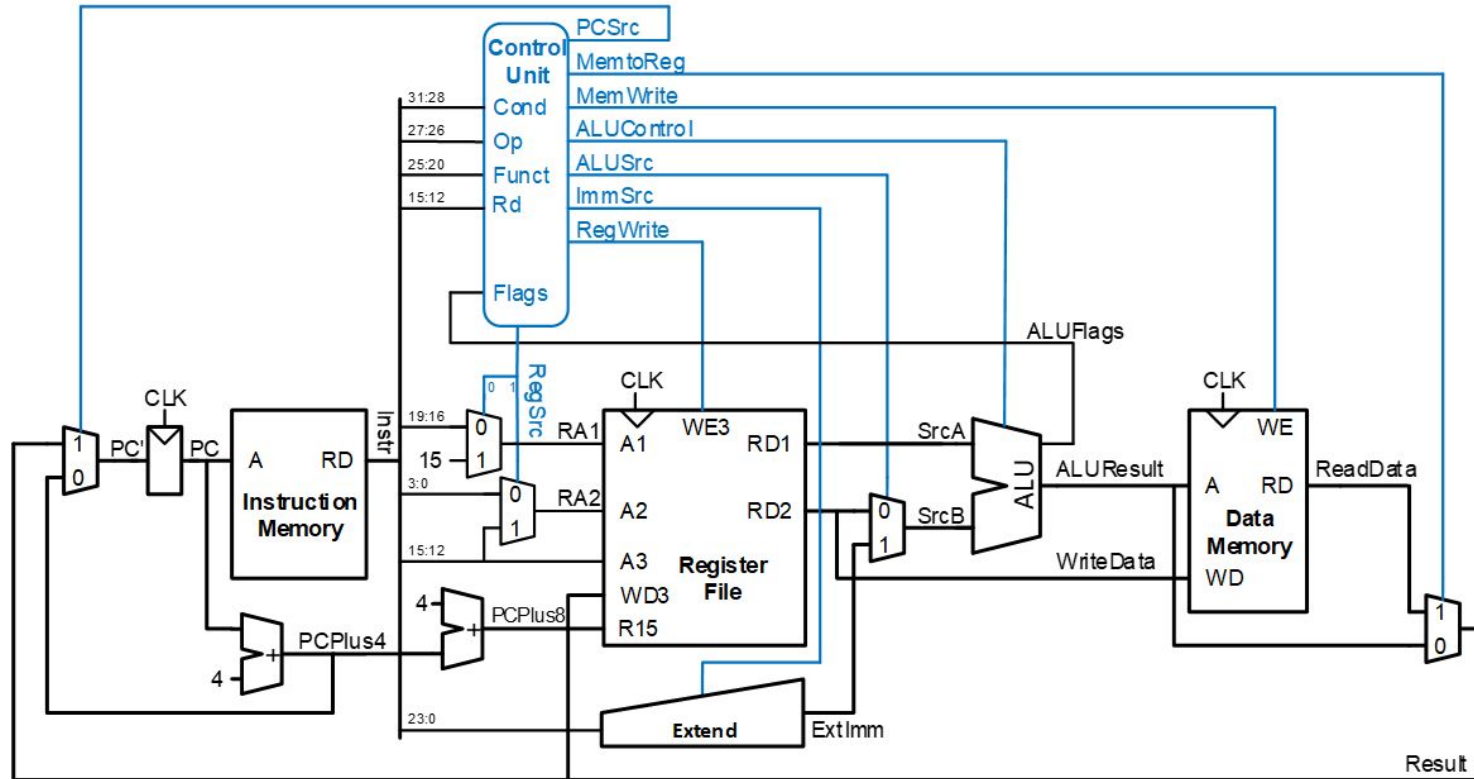


Recap Multicycle ARM Processor

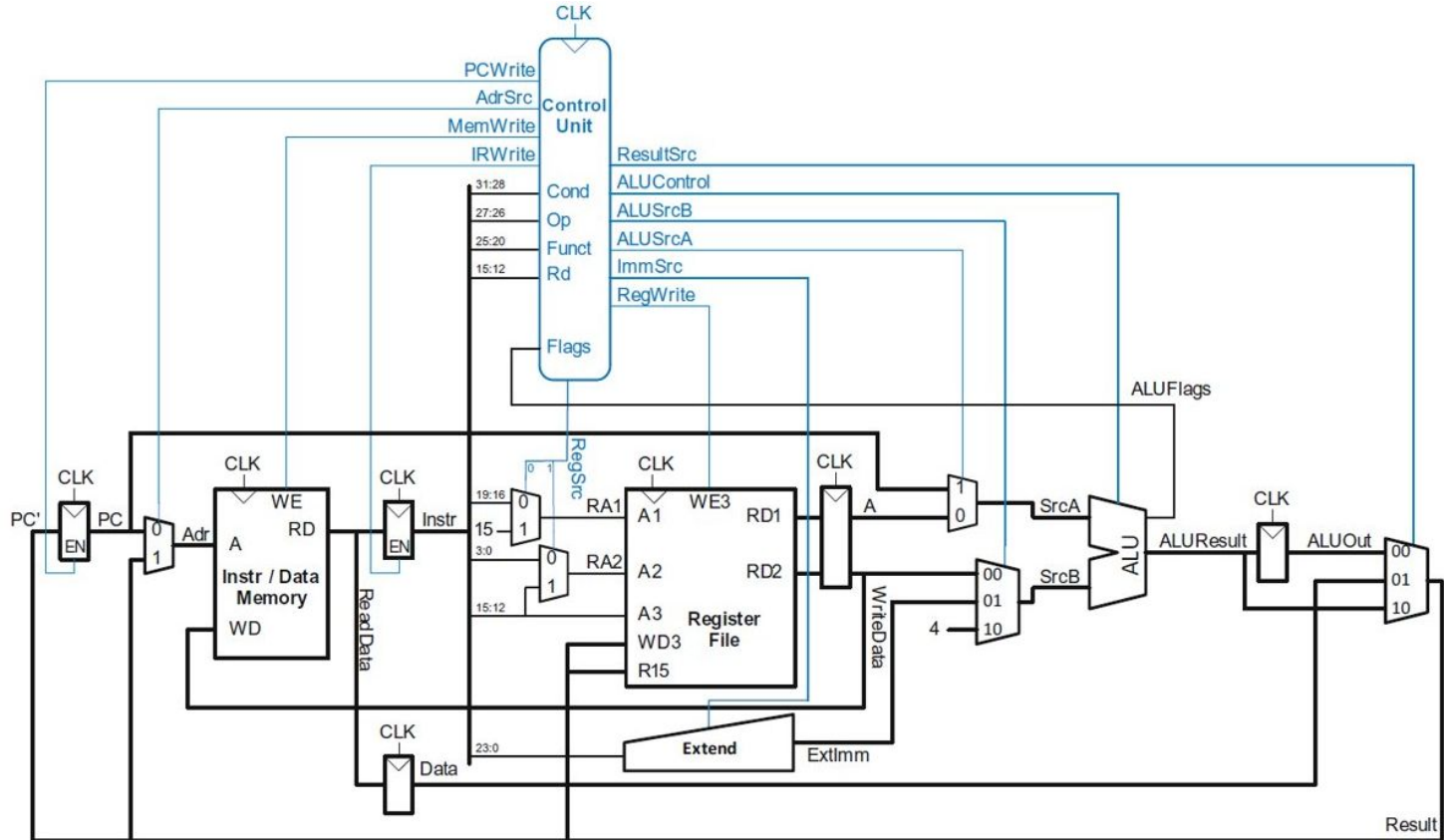

Side by Side

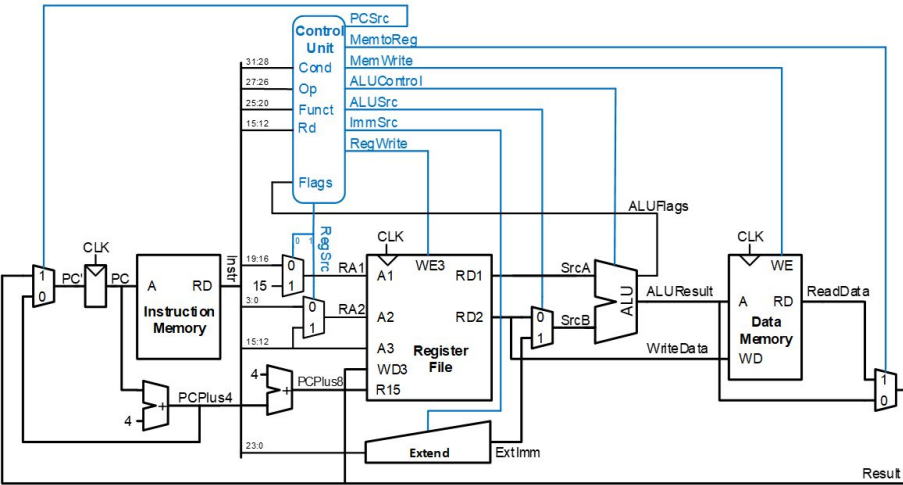

Single-Cycle

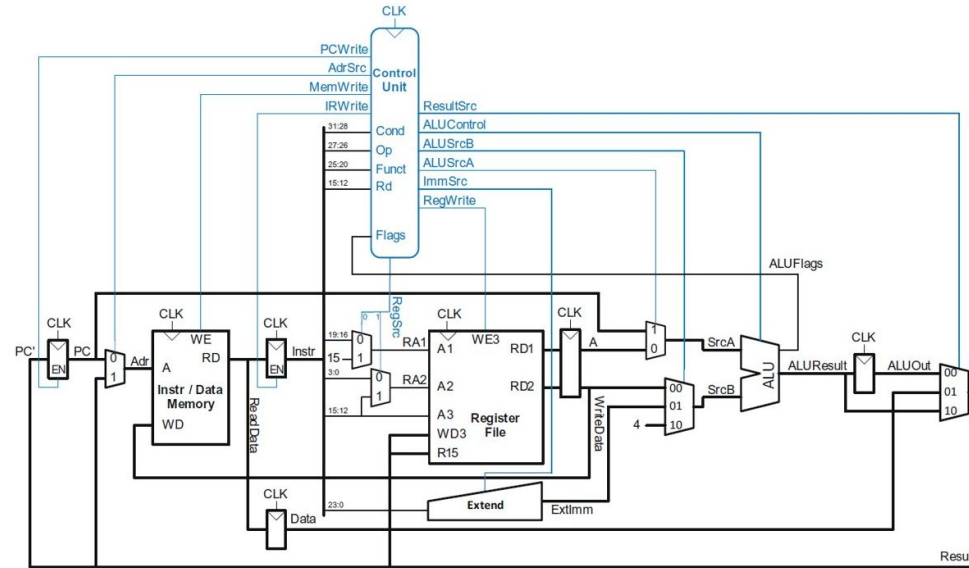

Multi-Cycle