



CPE 221: Computer Organization

14 Single Cycle ARM Processor
rahul.bhadani@uah.edu

Rahul Bhadani

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken up into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

Processor Performance

- Program execution time

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- Definitions:

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- Challenge is to satisfy constraints of:


- Cost
- Power
- Performance

- Consider **subset** of ARM instructions:
 - **Data-processing instructions:**
 - **ADD, SUB, AND, ORR**
 - with register and immediate Src2, but no shifts
 - **Memory instructions:**
 - **LDR, STR**
 - with positive immediate offset
 - **Branch instructions:**
 - **B**

Determines everything about a processor:

- Architectural state:
 - 16 registers (including PC)
 - Status register
- Memory

ARM Architectural State Elements

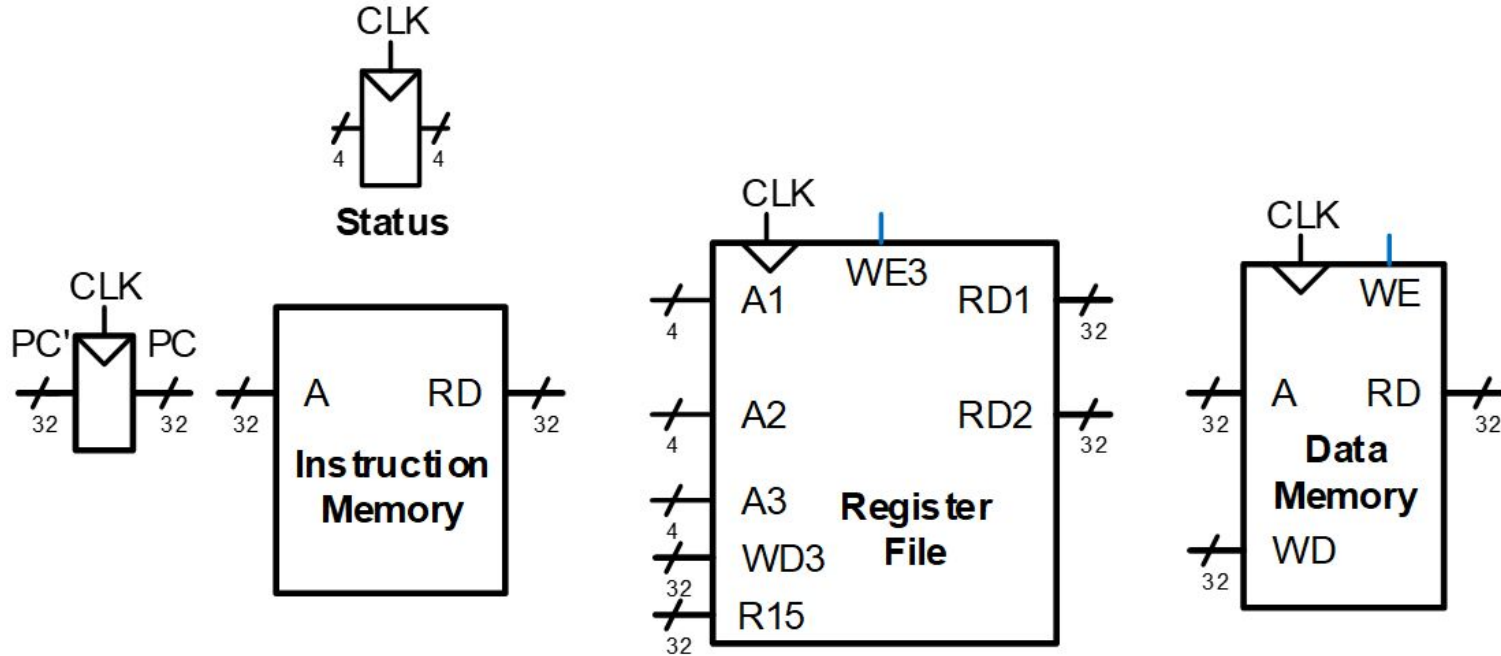

Single-Cycle ARM Processor


- Datapath
- Control

Single-Cycle ARM Processor

- Datapath: start with LDR instruction
- Example:


LDR R1, [R2, #5]

LDR Rd, [Rn, imm12]

 


Single-Cycle Datapath: LDR fetch

STEP 1: Fetch instruction

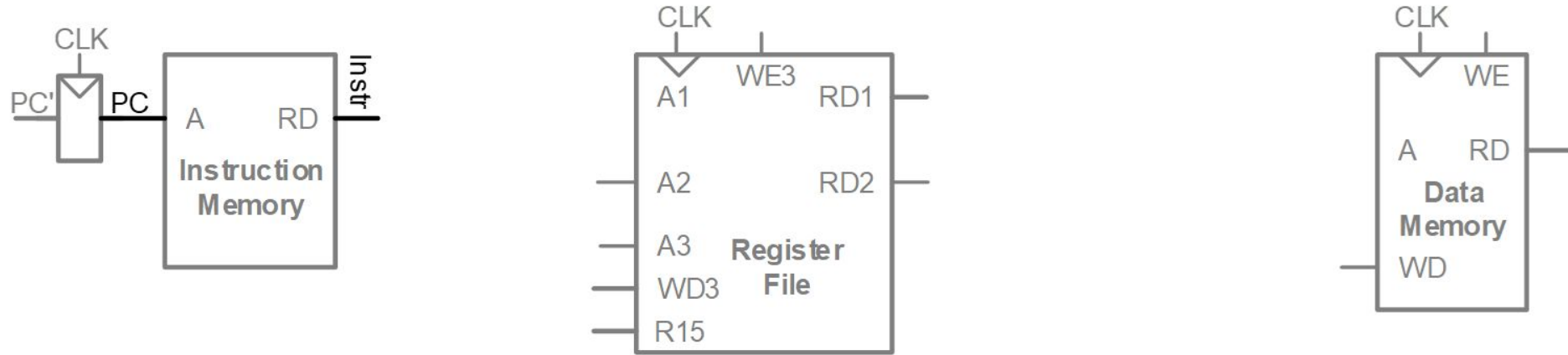


Single-Cycle Datapath: LDR Reg Read

STEP 2: Read source operands from RF

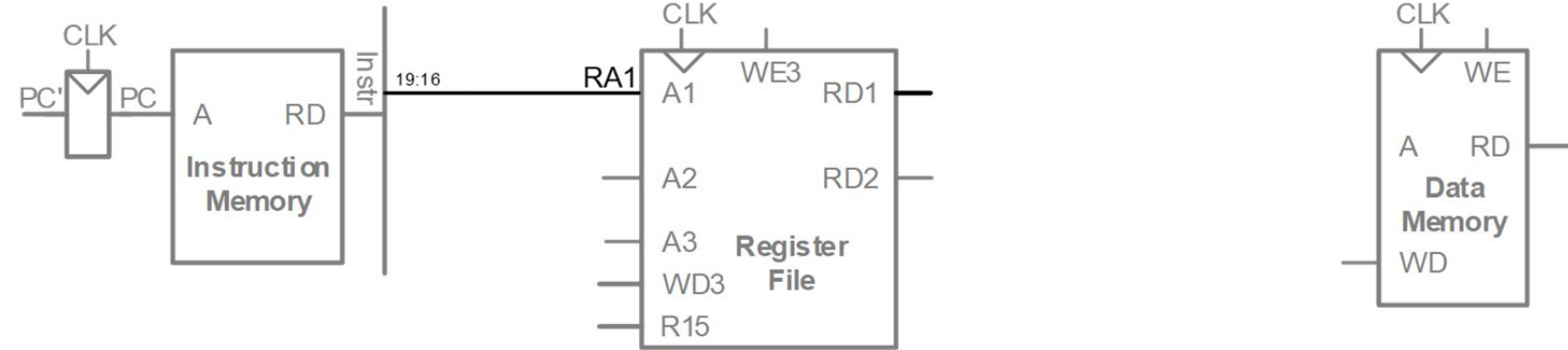

LDR Rd, [Rn, imm12]

Memory

 


Spring 2025

Spring 2025




Single-Cycle Datapath: LDR Address

STEP 4: Compute the memory address

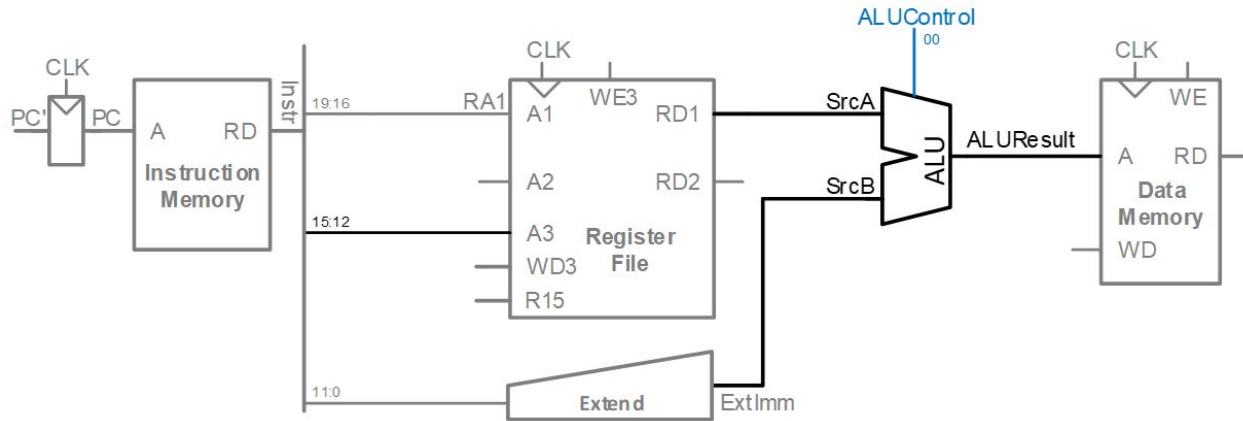


LDR Rd, [Rn, imm12]

 


Single-Cycle Datapath: LDR Mem Read

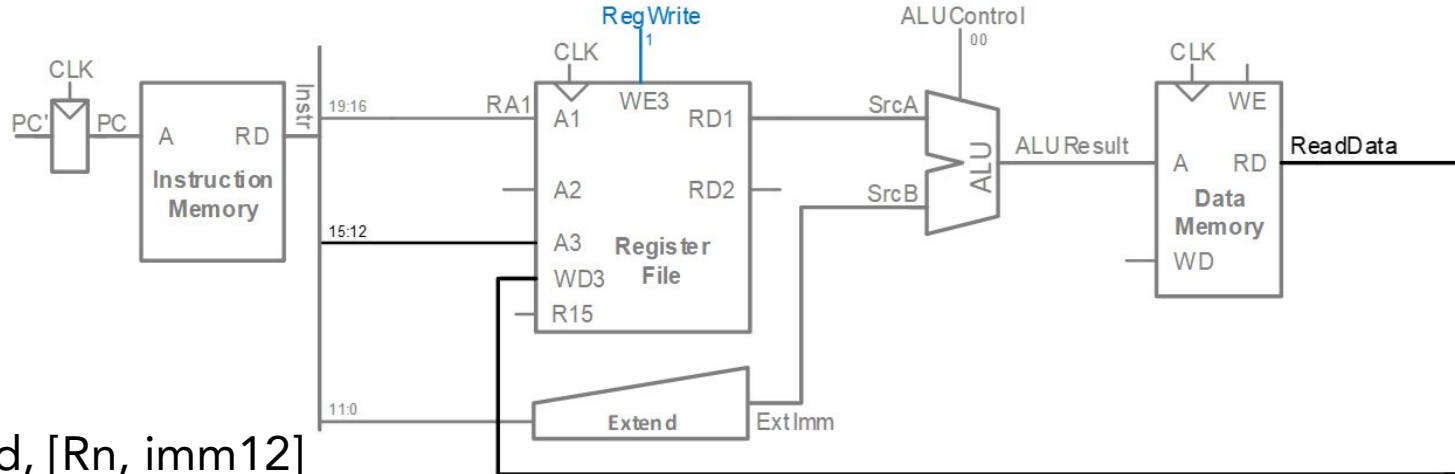STEP 5: Read data from memory and write it back to register file




LDR Rd, [Rn, imm12]

 

Single-Cycle Datapath: PC Increment

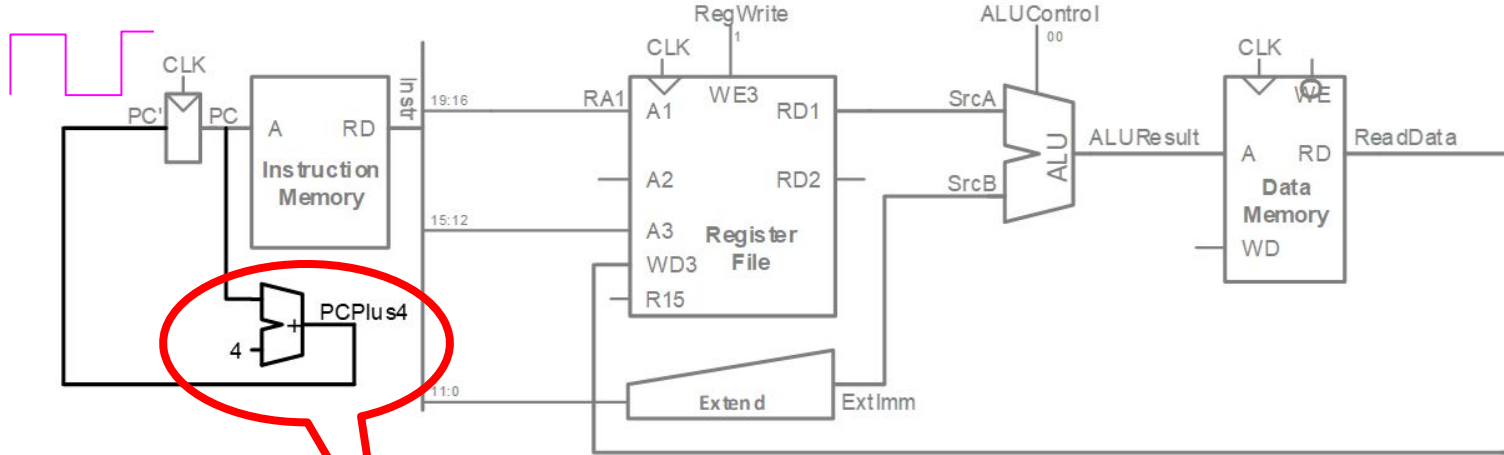
STEP 6: Determine address of next instruction



Calculate the address of the next instruction

Single-Cycle Datapath: Access to PC <Case of Destination being R15/PC>

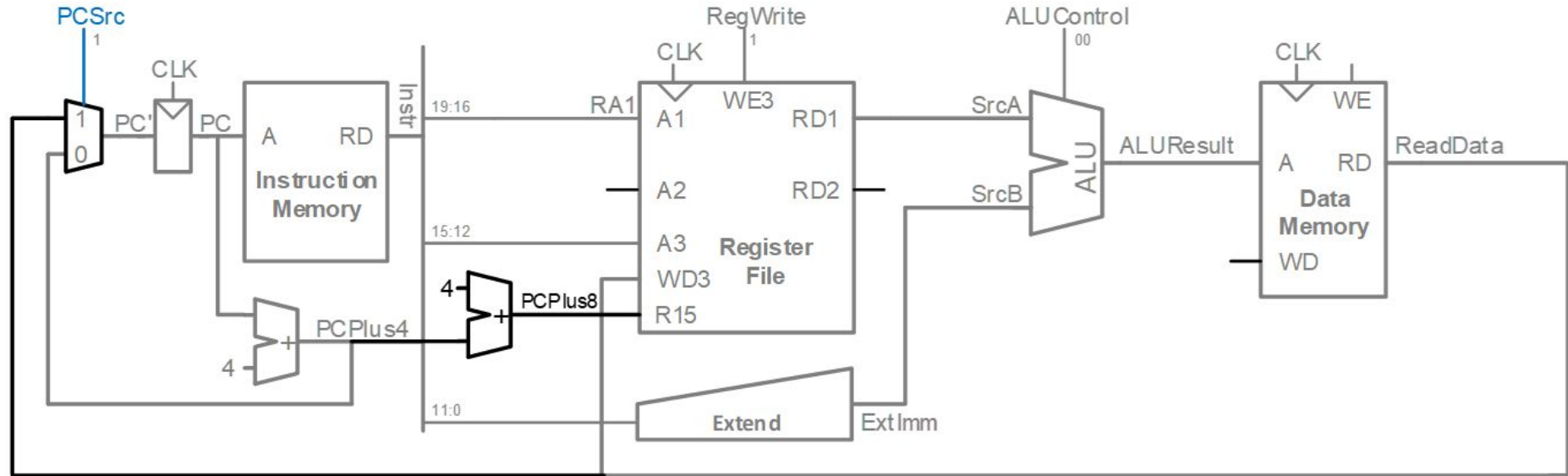
PC (R15) can be source/destination of instruction



Single-Cycle Datapath: Access to PC <Case of Destination being R15/PC>

PC can be source/destination of instruction

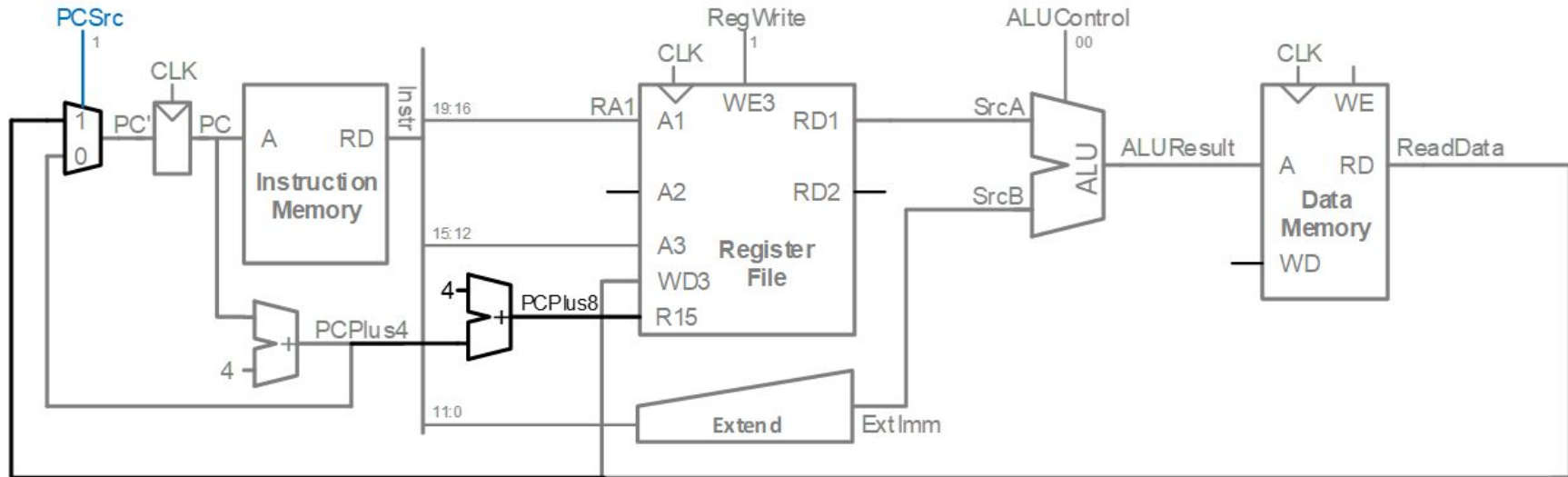
- **Source:** R15 must be available in Register File
 - PC is read as the current PC plus 8



Single-Cycle Datapath: Access to PC <Case of Destination being R15/PC>

PC can be source/destination of instruction


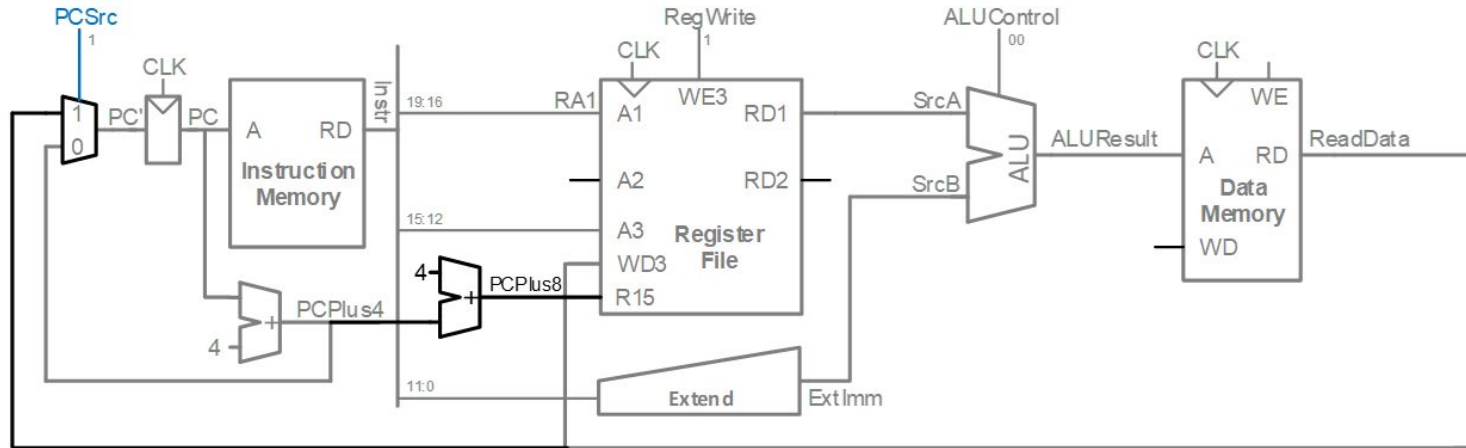
- **Source:** R15 must be available in Register File
 - PC is read as the current PC plus 8
- **Destination:** Be able to write result to PC



Single-Cycle Datapath: STR

Expand datapath to handle STR: STR Rd, [Rn, imm12]

- Write data in Rd to memory

 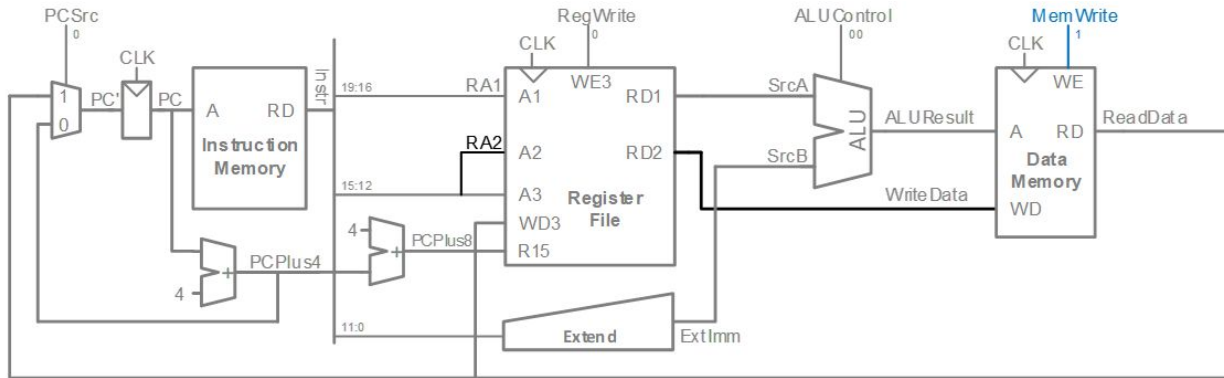


Single-Cycle Datapath: Data-processing

With **immediate** Src2:

- Read from Rn and Imm8 (*ImmSrc* chooses the zero-extended Imm8 instead of Imm12)
- Write *ALUResult* to register file
- Write to Rd

ADD Rd, Rn, imm8

 


Single-Cycle Datapath: Data-processing

With **immediate Src2**:

- Read from R_n and $Imm8$ ($ImmSrc$ chooses the zero-extended $Imm8$ instead of $Imm12$)
- Write $ALUResult$ to register file
- Write to R_d

ADD $R_d, R_n, imm8$

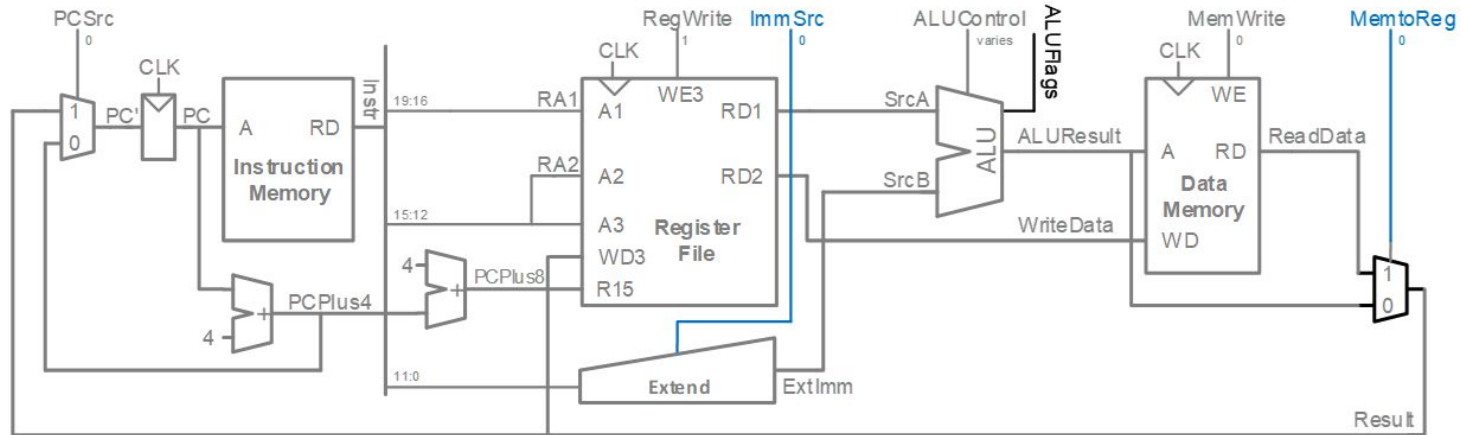



Single-Cycle Datapath: Data-processing

With **register** Src2:

- Read from Rn and Rm (instead of Imm8)
- Write *ALUResult* to register file
- Write to Rd

ADD Rd, Rn, Rm

Data-processing

  


Single-Cycle Datapath: Data-processing

With **register Src2**:

- Read from Rn and Rm (instead of Imm8)
- Write *ALUResult* to register file
- Write to Rd

**Same ALU handles, ADD (00),
SUB(01), AND (10), ORR (11)**

ADD Rd, Rn, Rm

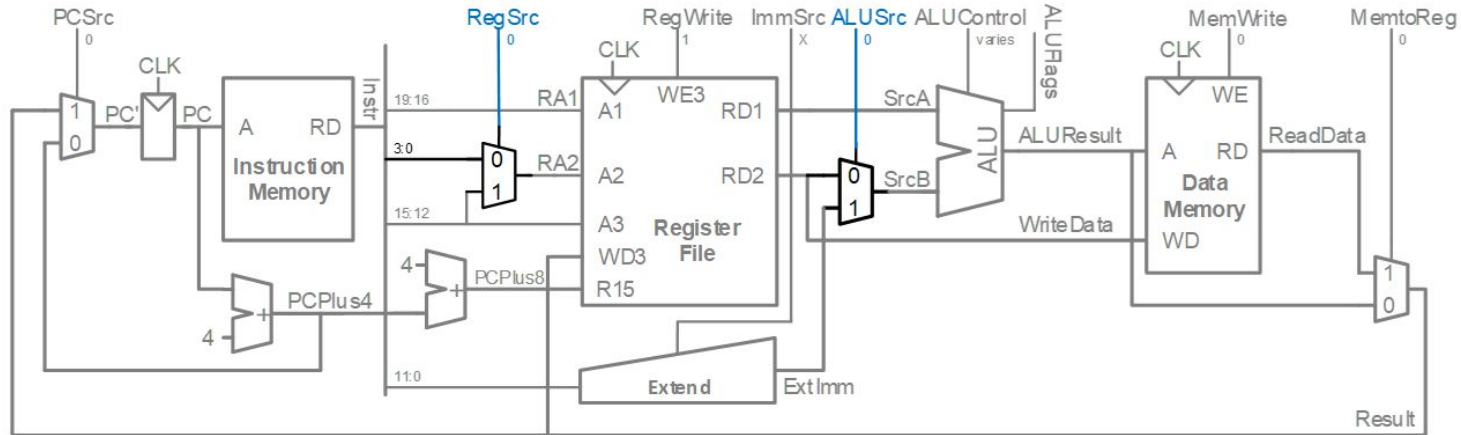


Single-Cycle Datapath: B

Calculate branch target address:


$$\text{BTA} = (\text{ExtImm}) + (\text{PC} + 8)$$

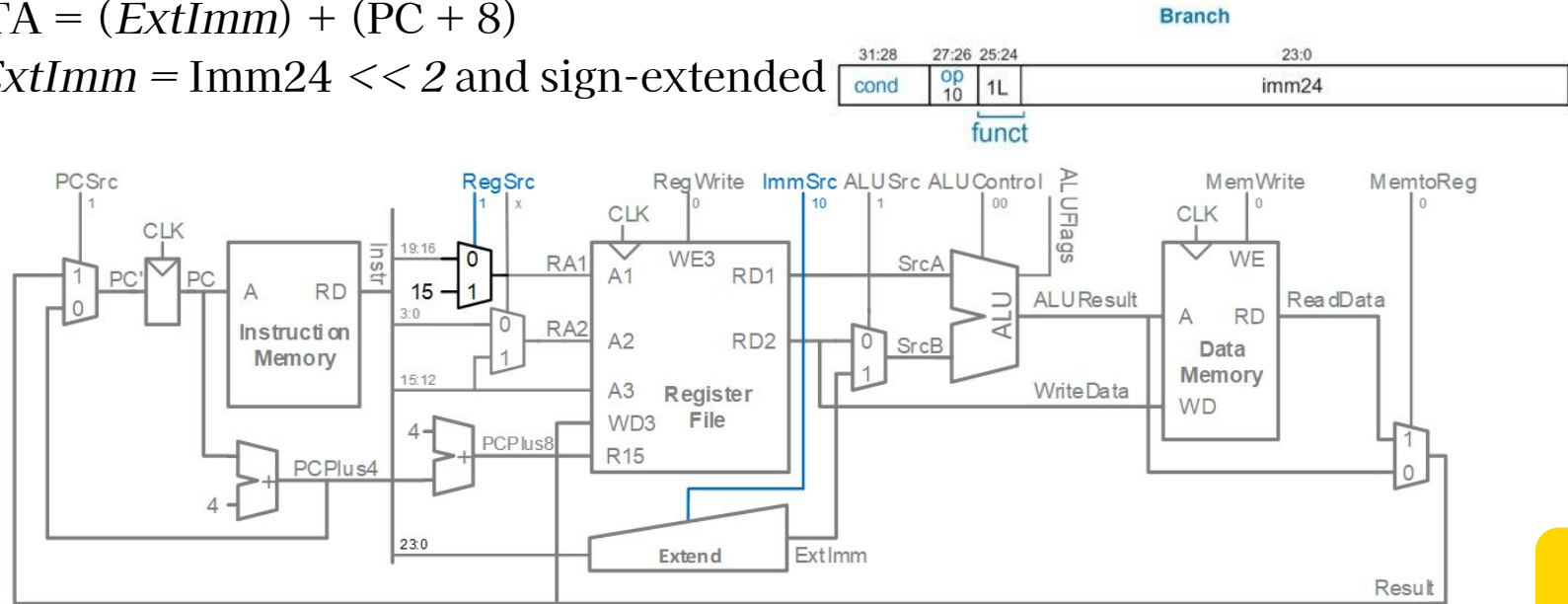$\text{ExtImm} = \text{Imm24} \ll 2$ and sign-extended




Single-Cycle Datapath: ExtImm


ImmSrc _{1:0}	ExtImm	Description
00	{24 0s, Instr _{7:0} }	Zero-extended <i>imm8</i>
01	{20 0s, Instr _{11:0} }	Zero-extended <i>imm12</i>
10	{6 Instr ₂₃ }, Instr _{23:0} }	Sign-extended <i>imm24</i>

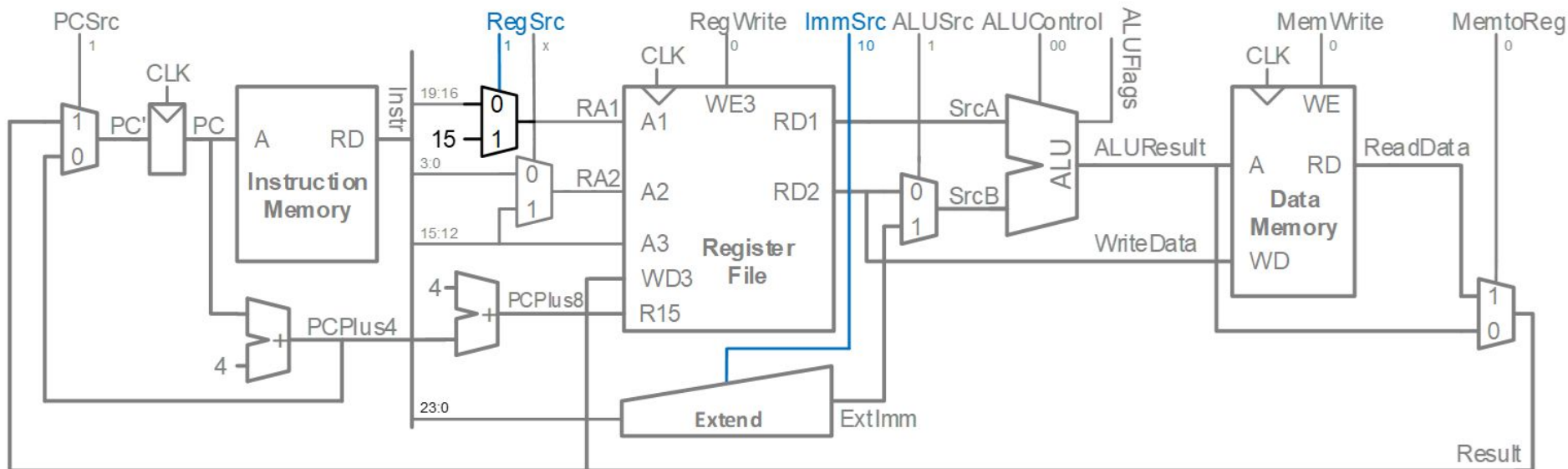


Single-Cycle ARM Processor

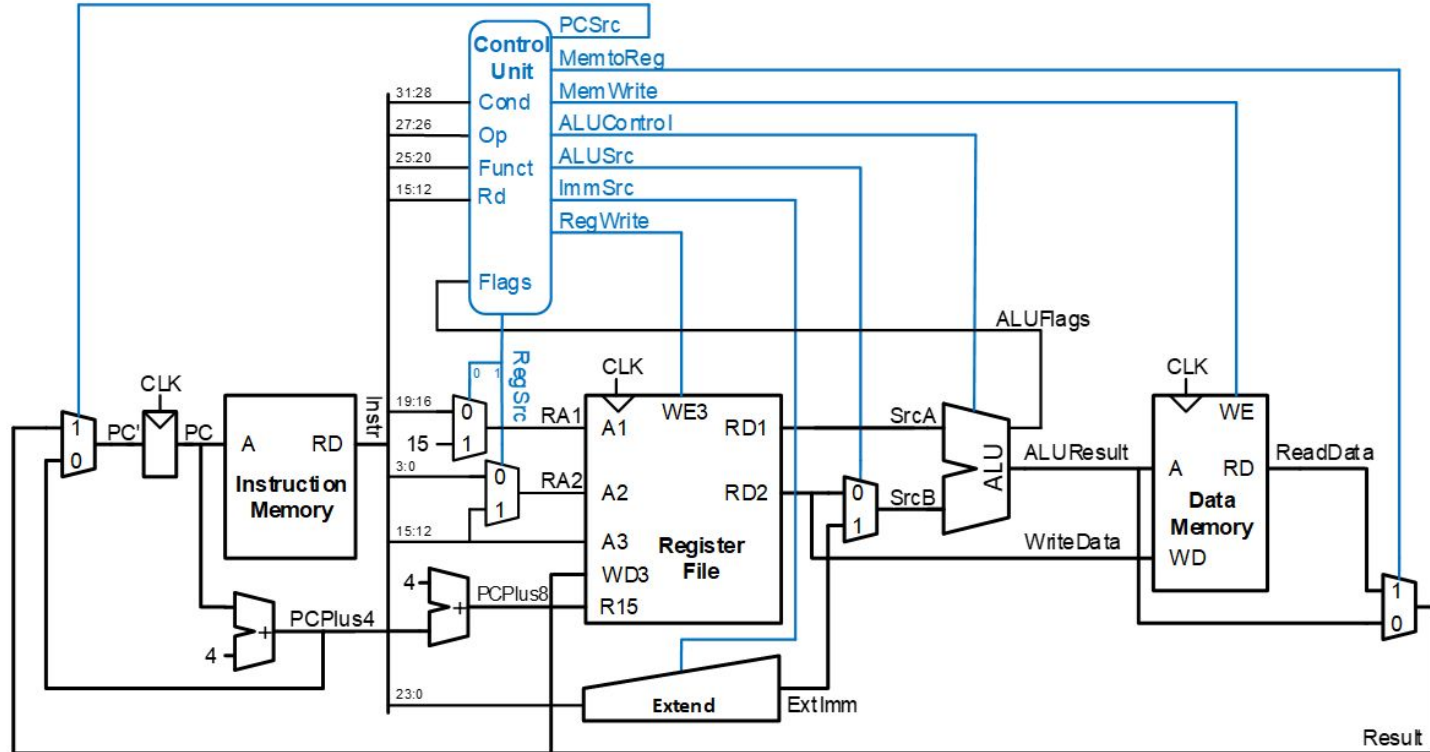


Single-Cycle Control

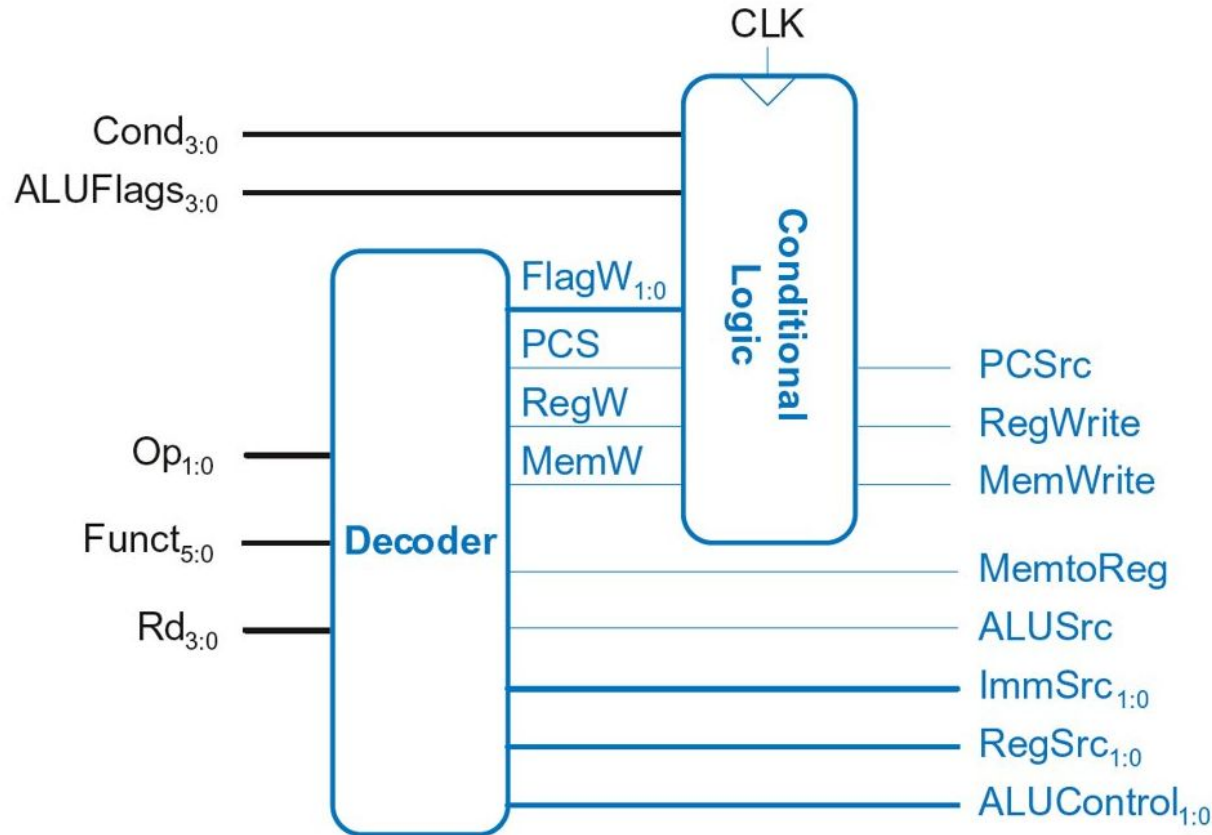


Single-Cycle Control

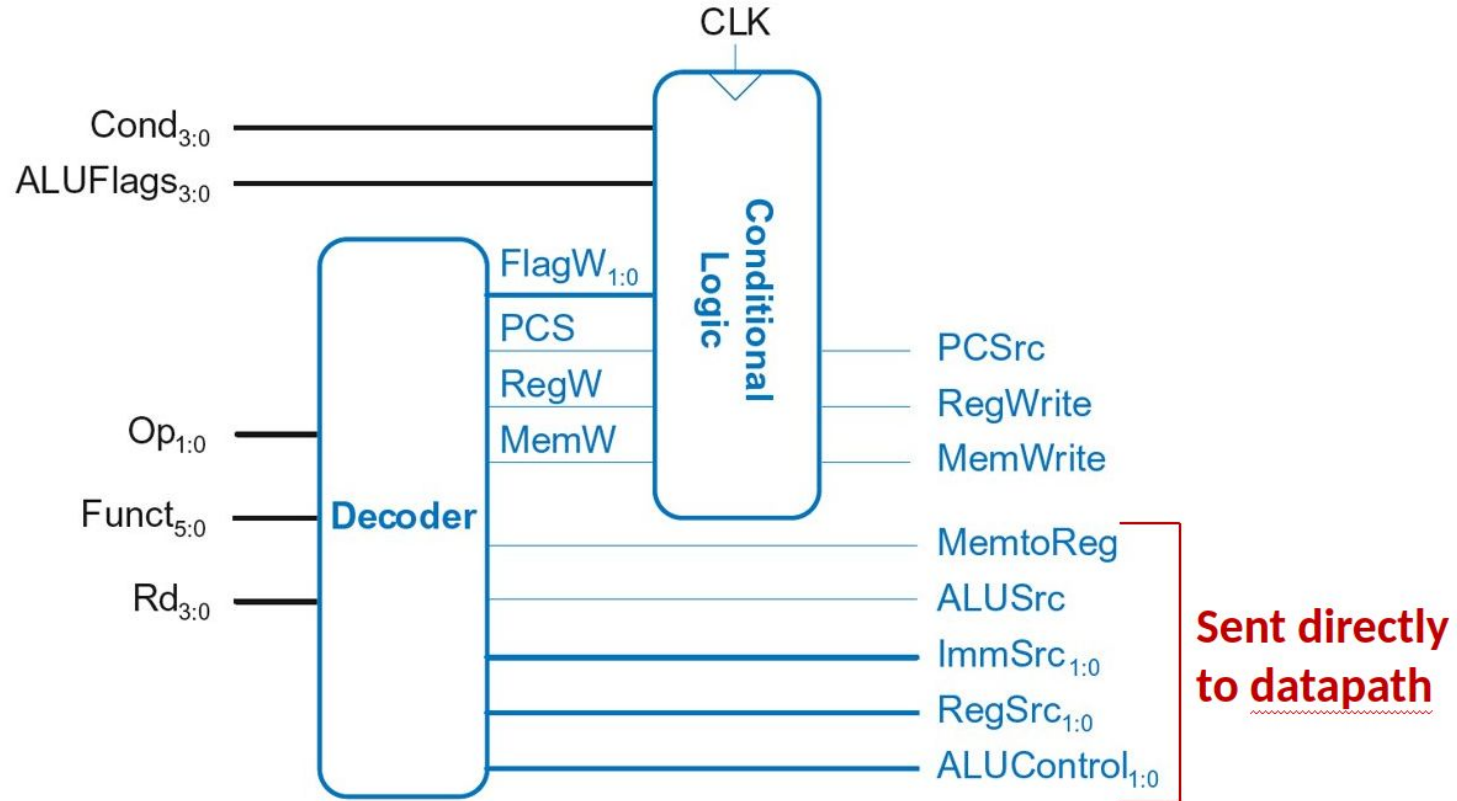


Single-Cycle Control

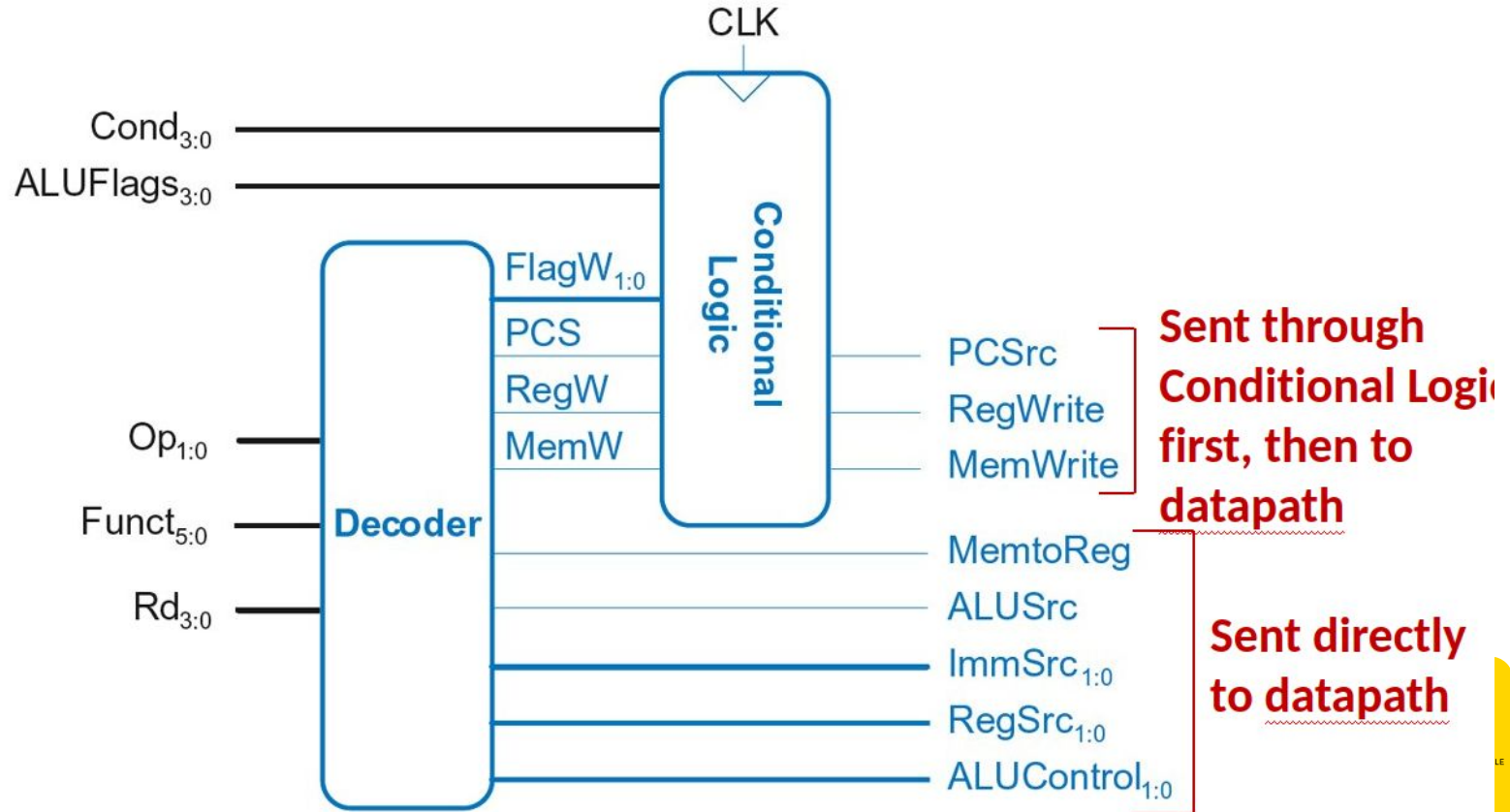

Single-Cycle Control

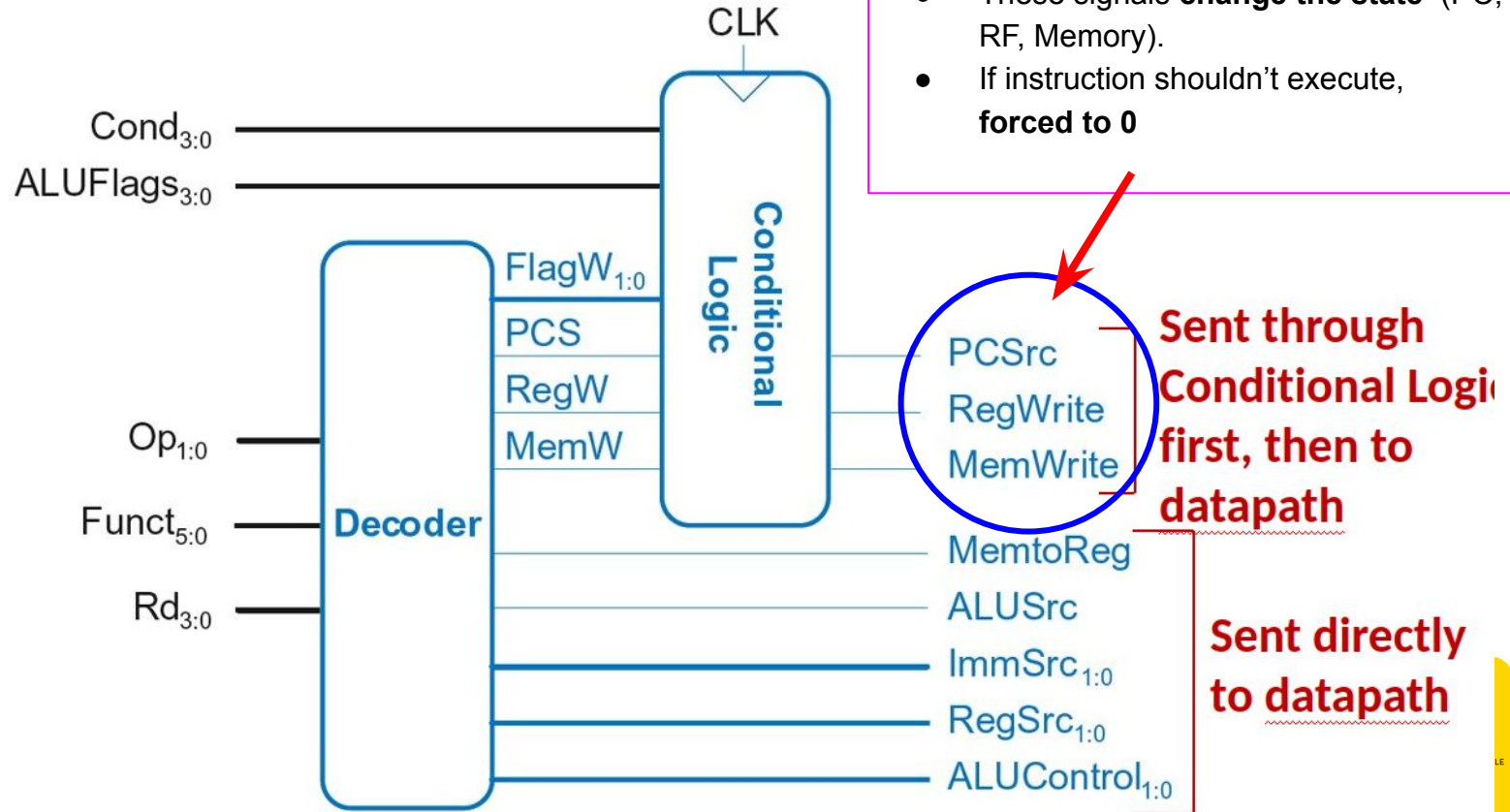


Single-Cycle Control

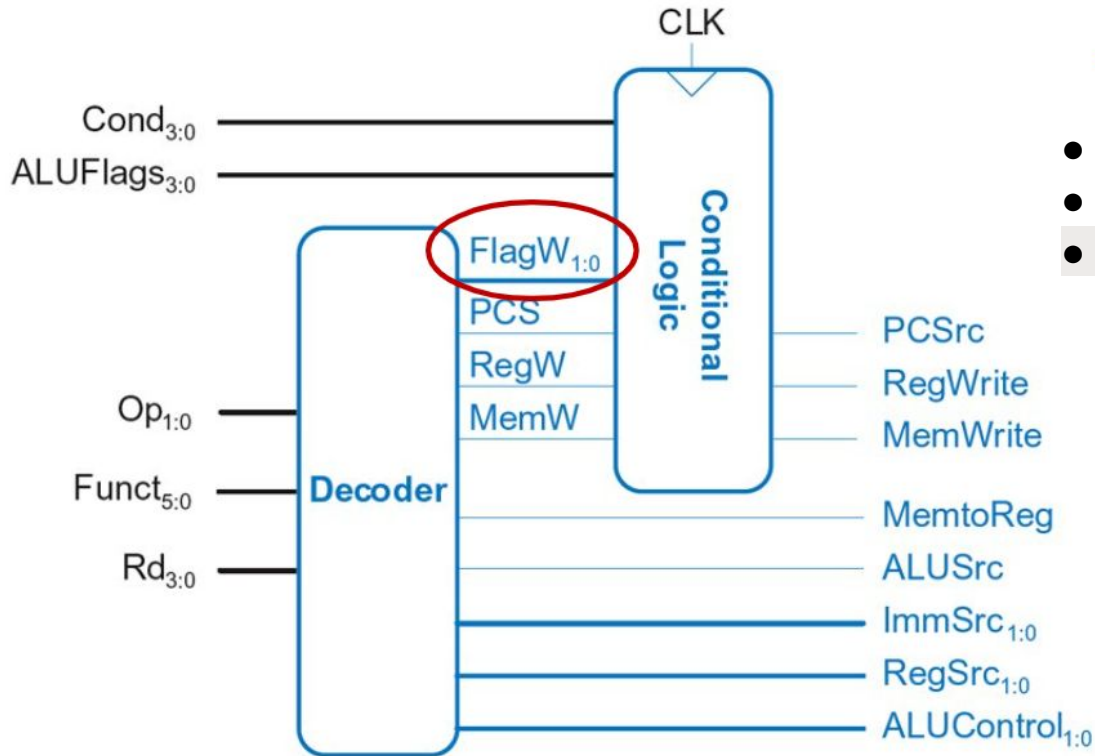


- **$FlagW_{1:0}$:** Flag Write signal, asserted when $ALUFlags$ should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (NZCV)
- AND, ORR only update NZ flags
- So, two bits needed:
 - $FlagW_1$** = 1: NZ saved ($ALUFlags_{3:2}$ saved)
 - $FlagW_0$** = 1: CV saved ($ALUFlags_{1:0}$ saved)

Single-Cycle Control

 


Single-Cycle Control: Decoder

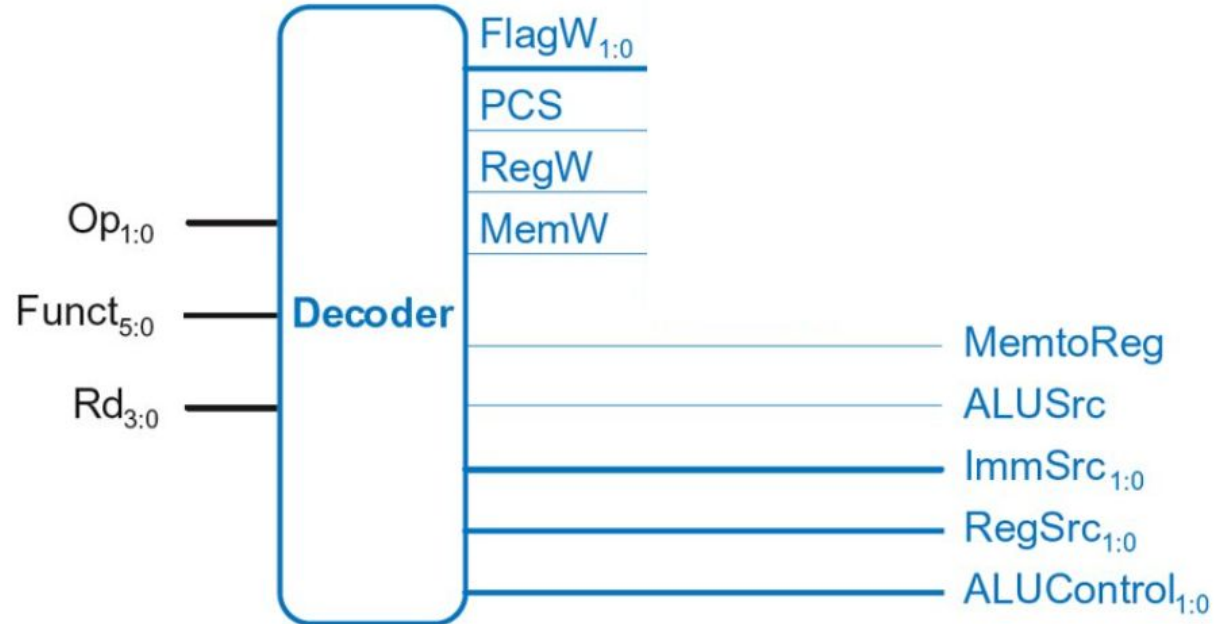

Single-Cycle Control: Decoder

Submodules:

- Main Decoder
- ALU Decoder
- PC Logic

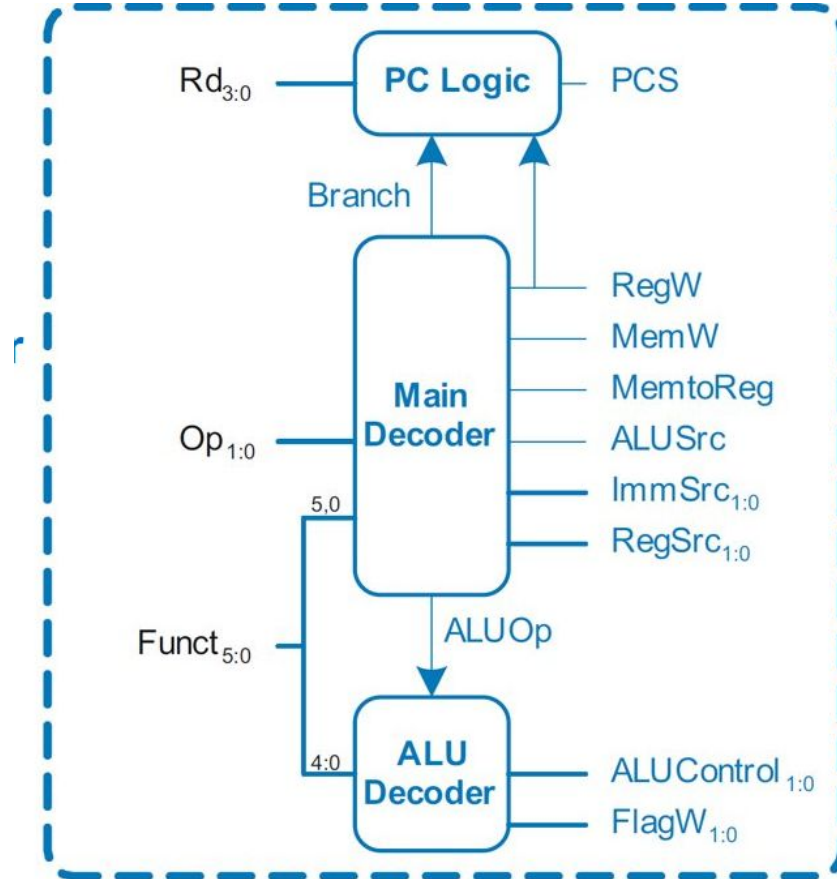


Control Unit: Main Decoder

Op	Func ₅	Func ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
11	X	X	B	1	0	0	1	10	0	X1	0

Single-Cycle Control: Decoder


Submodules:

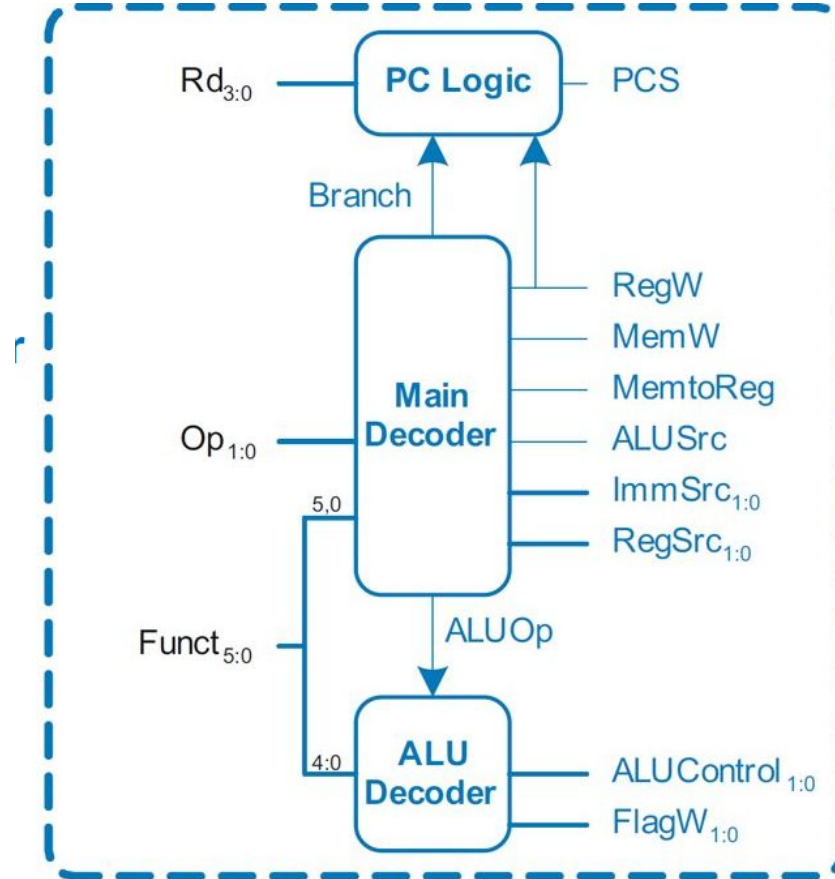- Main Decoder
- **ALU Decoder**
- PC Logic



Review: ALU

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

 




Single-Cycle Control: Decoder

Submodules:

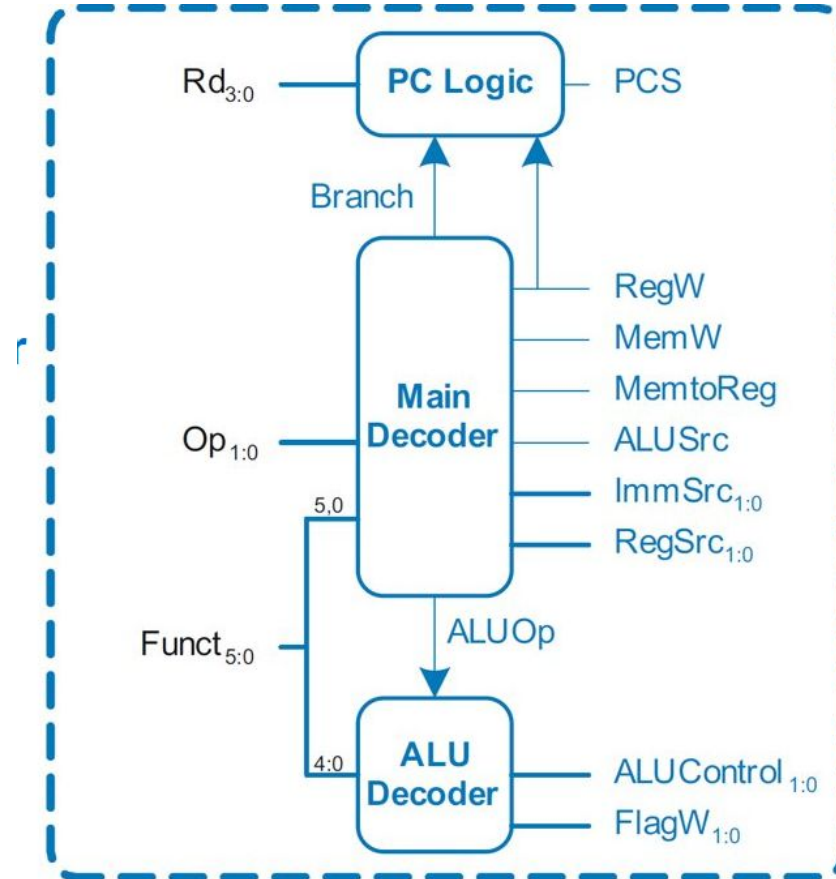- Main Decoder
- **ALU Decoder**
- PC Logic



Control Unit: ALU Decoder


- **FlagW_h** = 1: *NZ* (*Flags*_{3:2}) should be saved
- **FlagW₀** = 1: *CV* (*Flags*_{1:0}) should be saved

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

Single-Cycle Control: Decoder

Submodules:

- Main Decoder
- ALU Decoder
- PC Logic

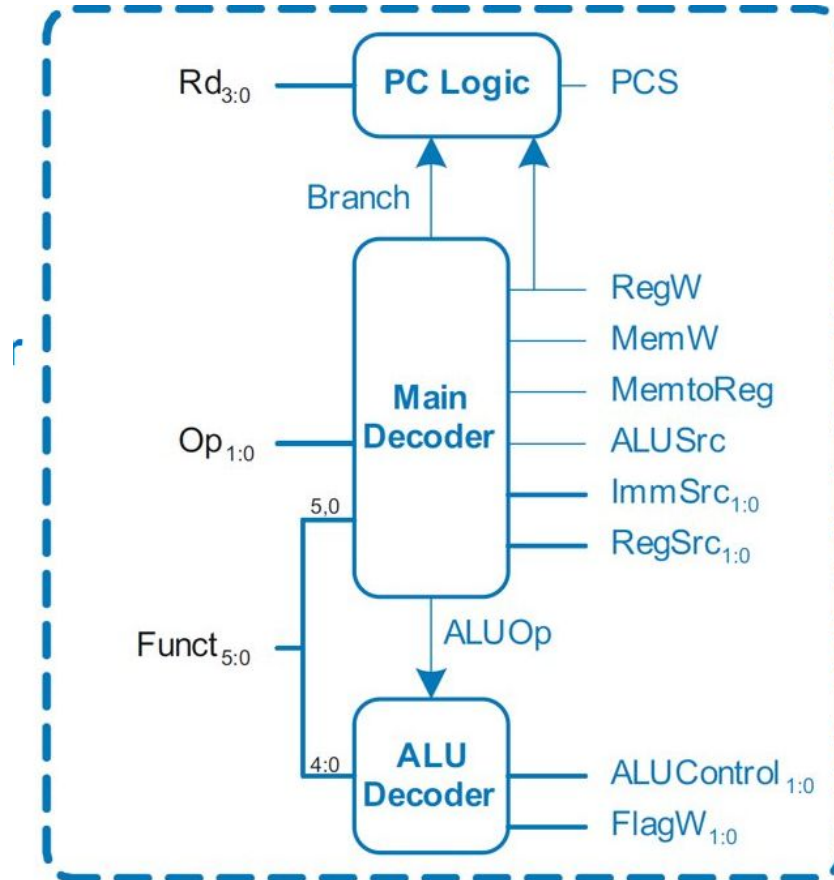


Single-Cycle Control: PC Logic

PCSrc = 1 if PC is written by an instruction or branch (B):


$$PCSrc = ((Rd == 15) \& RegW) \mid Branch$$

If instruction is executed: $PCSrc = PCSrc$

Else $PCSrc = 0$ (i.e., $PC = PC + 4$)

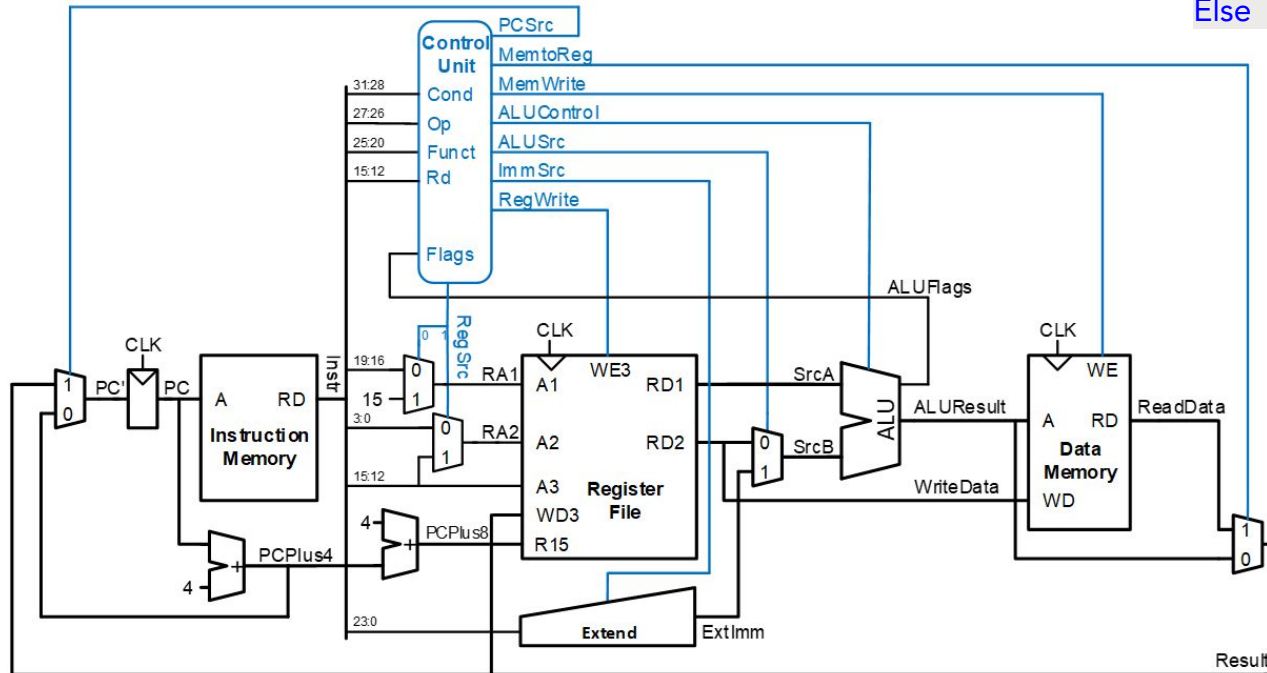


Single-Cycle Control: Cond. Logic

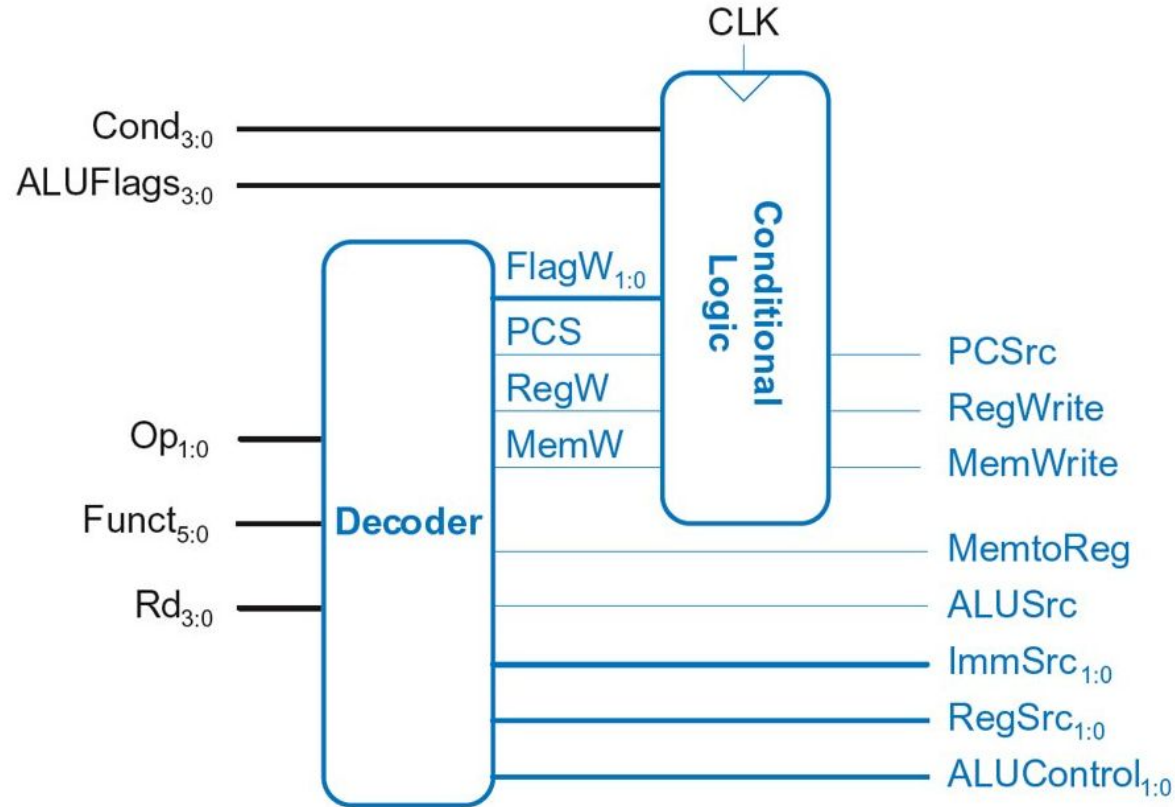

Single-Cycle Control: Cond. Logic

Function:

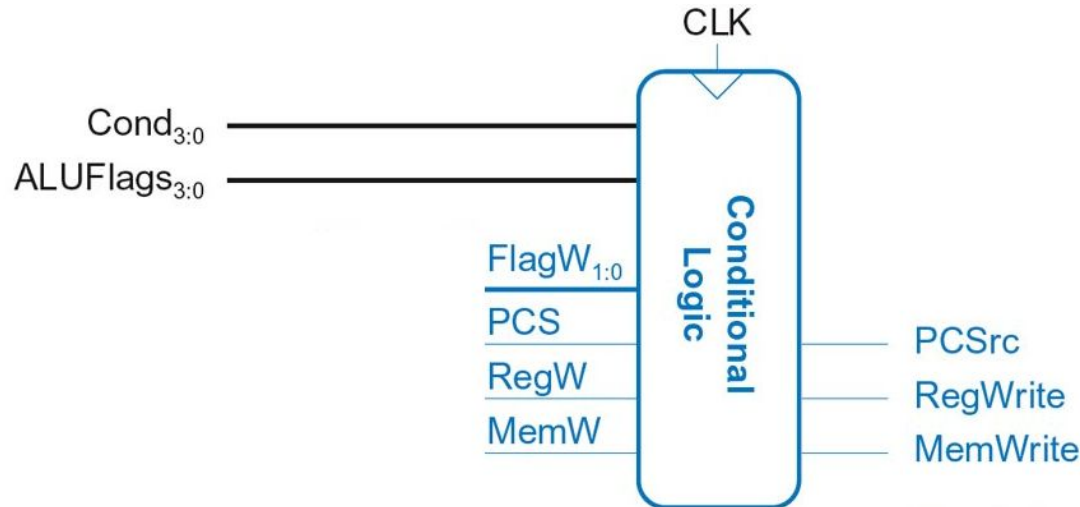
1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags_{3:0})



Single-Cycle Control: Cond. Logic

Function:

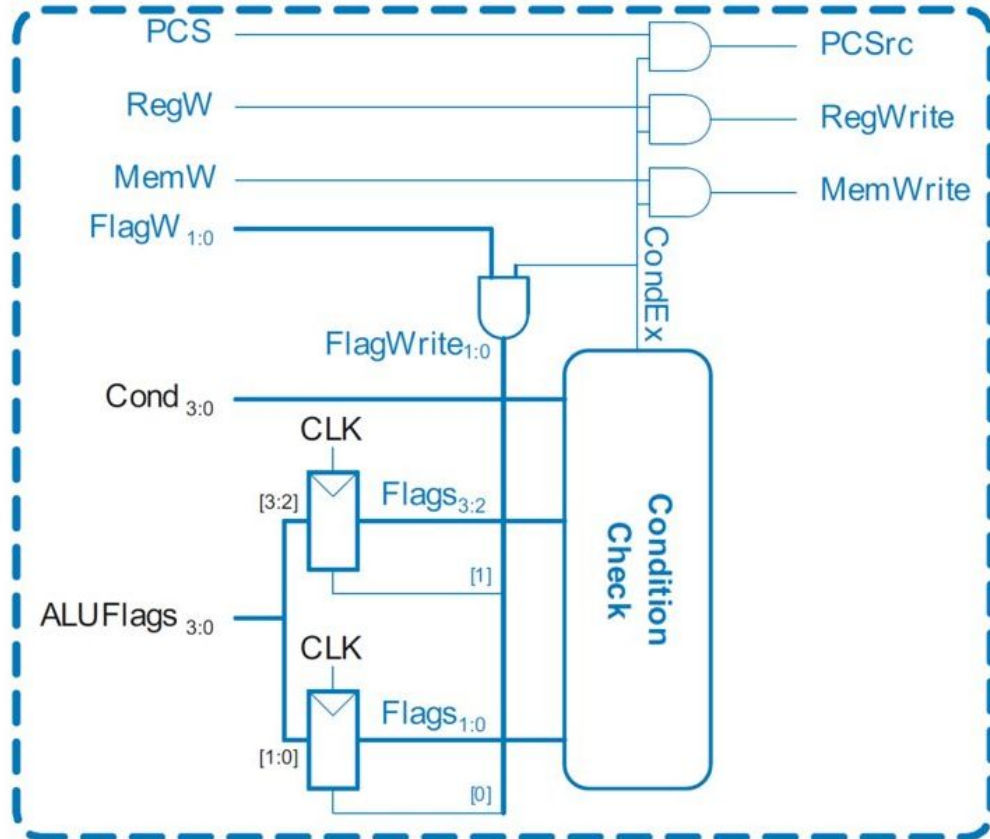1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)




Single-Cycle Control: Cond. Logic

Flags_{3:0} is the status register

Function:

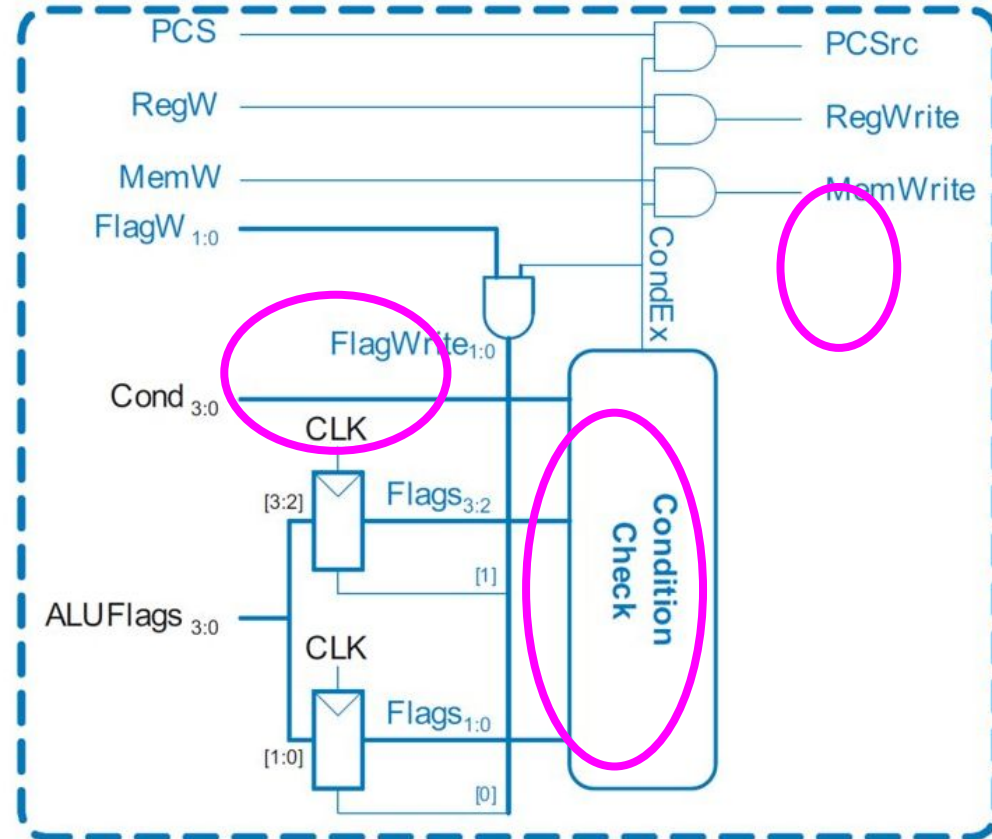1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)

Depending on condition mnemonic ($Cond_{3:0}$) and condition flags ($Flags_{3:0}$) the instruction is executed ($CondEx = 1$)



Review: Condition Mnemonics

Cond _{3:0}	Mnemonic	Name	CondEx
0000	EQ	Equal	
0001	NE	Not equal	
0010	CS / HS	Carry set / Unsigned higher or same	
0011	CC / LO	Carry clear / Unsigned lower	
0100	MI	Minus / Negative	
0101	PL	Plus / Positive of zero	
0110	VS	Overflow / Overflow set	
0111	VC	No overflow / Overflow clear	
1000	HI	Unsigned higher	
1001	LS	Unsigned lower or same	
1010	GE	Signed greater than or equal	
1011	LT	Signed less than	
1100	GT	Signed greater than	
1101	LE	Signed less than or equal	
1110	AL (or none)	Always / unconditional	ignored

Conditional Logic: Conditional Execution


Example:

AND R1, R2, R3

Cond_{3:0}=1110 (unconditional) =>

CondEx = 1

Flags_{3:0} is the status register

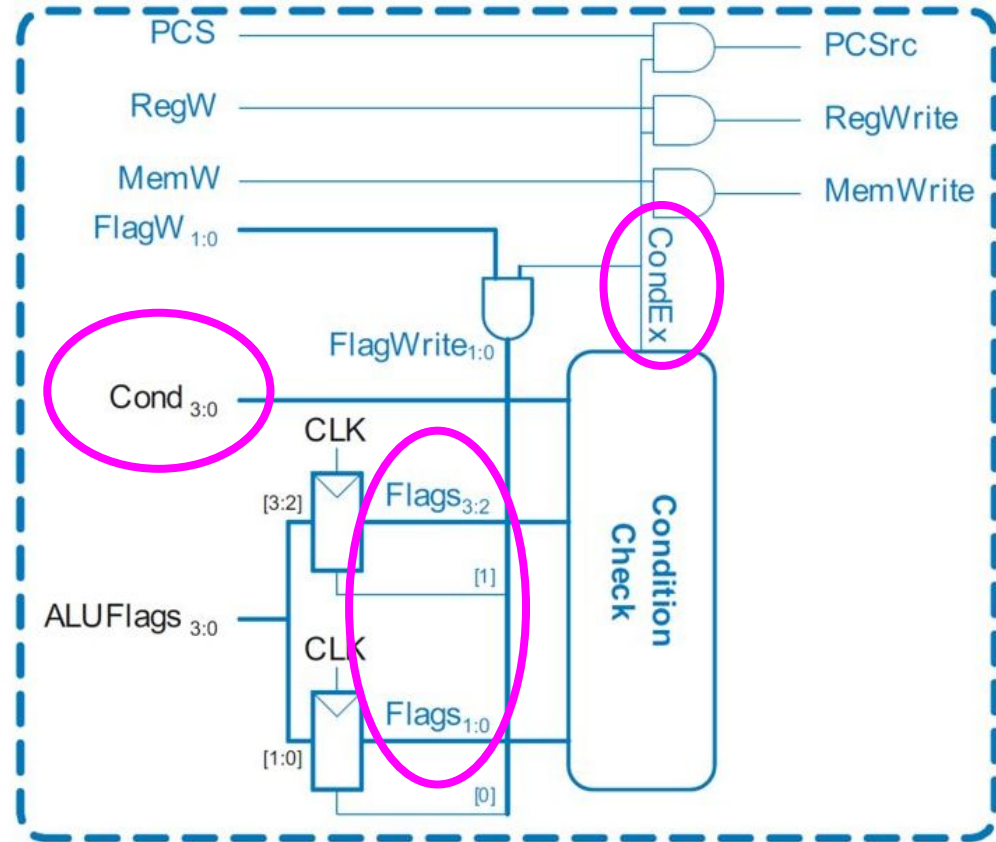

Conditional Logic: Conditional Execution

Example:


EOREQ R5, R6, R7

Cond_{3:0}=0000 (EQ): if

Flags_{3:2}=0100 => **CondEx** =


1

Flags_{3:0} is the status register

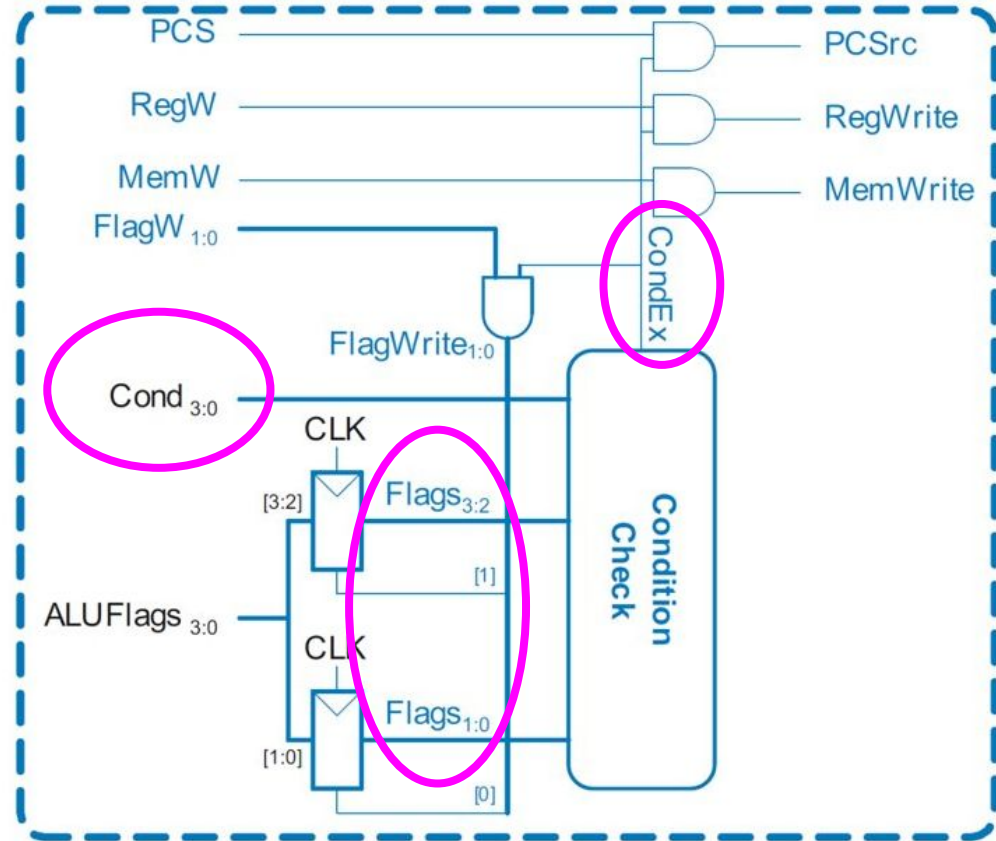

Function:


2. Possibly update Status Register (Flags_{3:0})

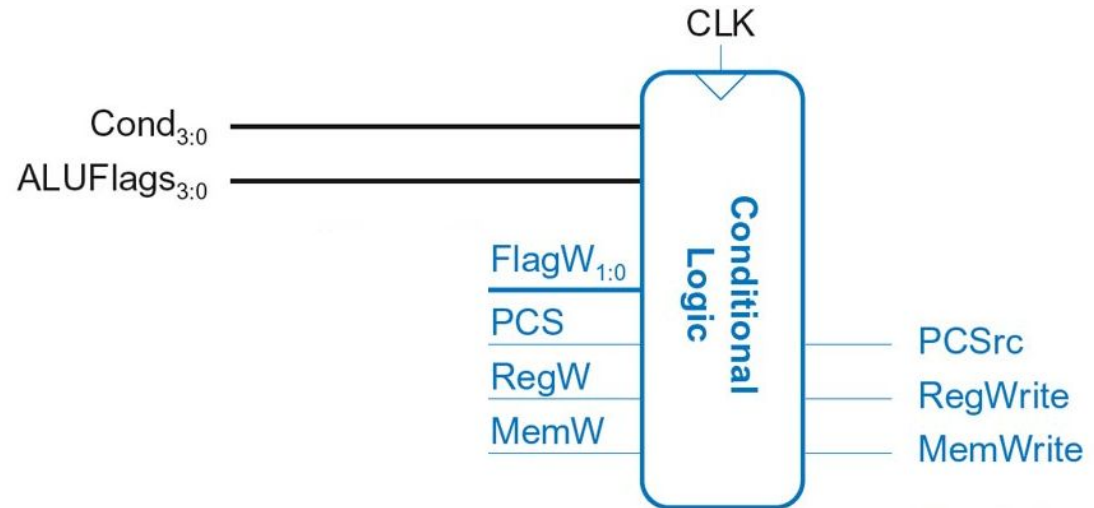

Flags3:0 is the status register

Flags_{3:0} updated (with ALUFlags_{3:0})
if:

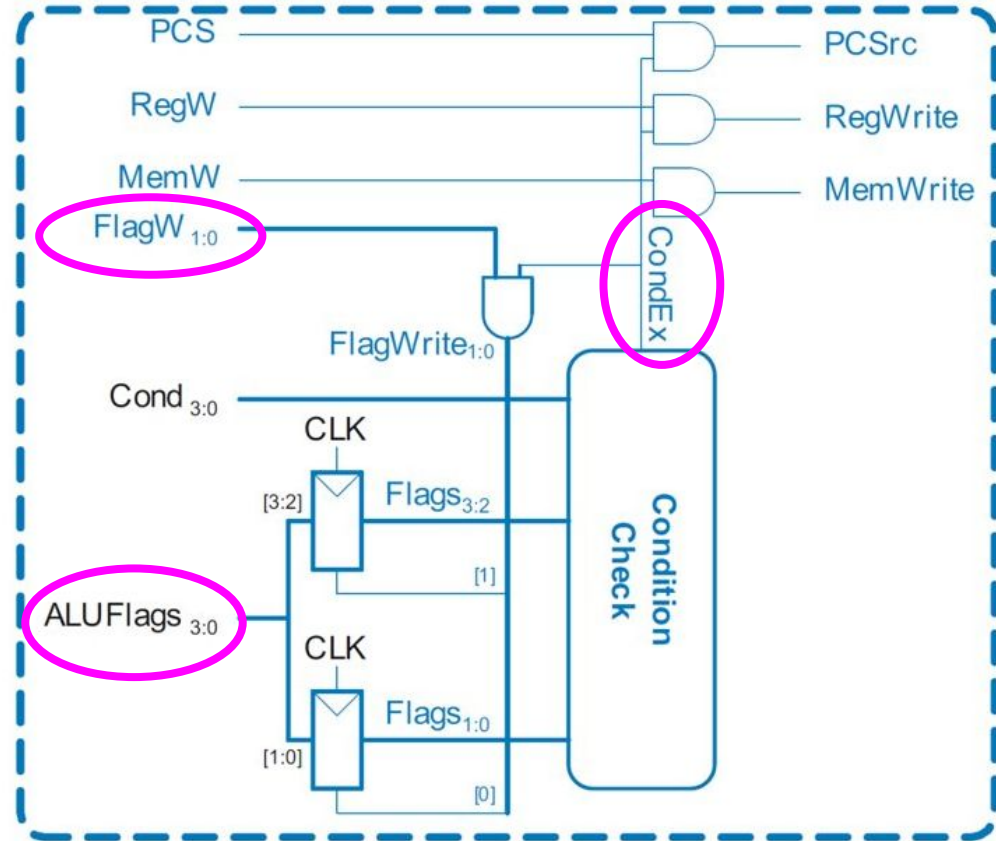
- **FlagW** is 1 (i.e., the instruction's S-bit is 1) AND
- **CondEx** is 1 (the instruction should be executed)



Conditional Logic: Update (Set) Flags

Recall:

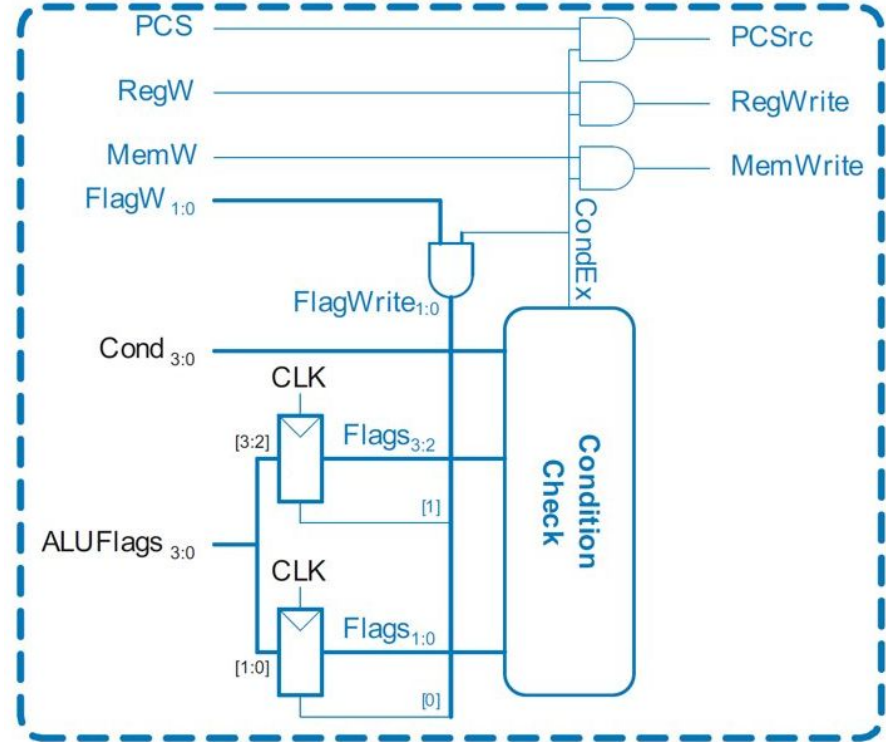- ADD, SUB update **all** Flags
- AND, OR update **NZ only**
- So Flags status register has two write enables: **FlagW1:0**



Review: ALU Decoder

- $FlagW_1 = 1$: NZ ($Flags_{3:2}$) should be saved
- $FlagW_0 = 1$: CV ($Flags_{1:0}$) should be saved

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10


Single-Cycle Control: Cond. Logic

Flags_{3:0} is the **status register**

Example: SUBS R5, R6, R7

FlagW_{1:0} = 11 AND CondEx = 1 (unconditional) => FlagWrite_{1:0} = 11

All Flags updated

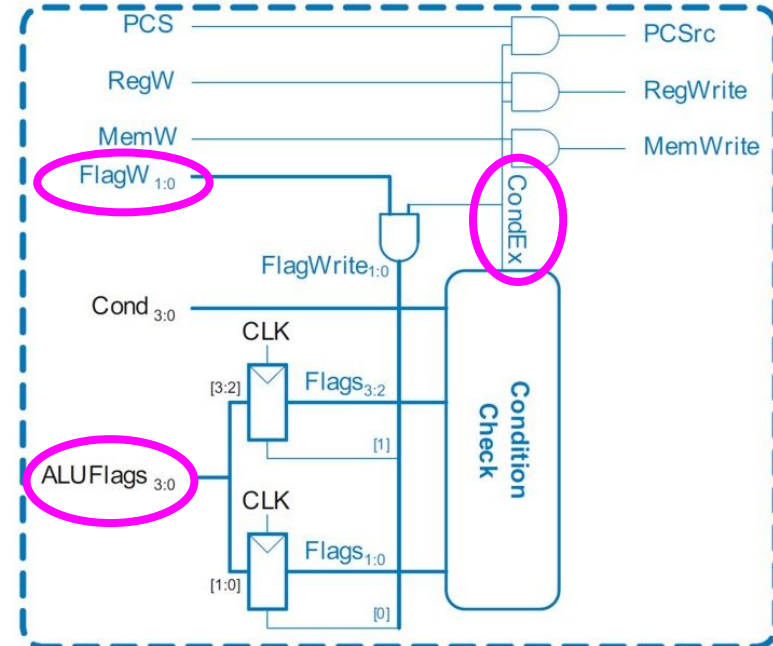

Single-Cycle Control: Cond. Logic


Flags_{3:0} is the **status register**

Example: ANDS R7, R1, R3

FlagW_{1:0} = 10 AND **CondEx** = 1 (unconditional) => **FlagWrite**_{1:0} = 10


Flags_{3:0} = NZCV

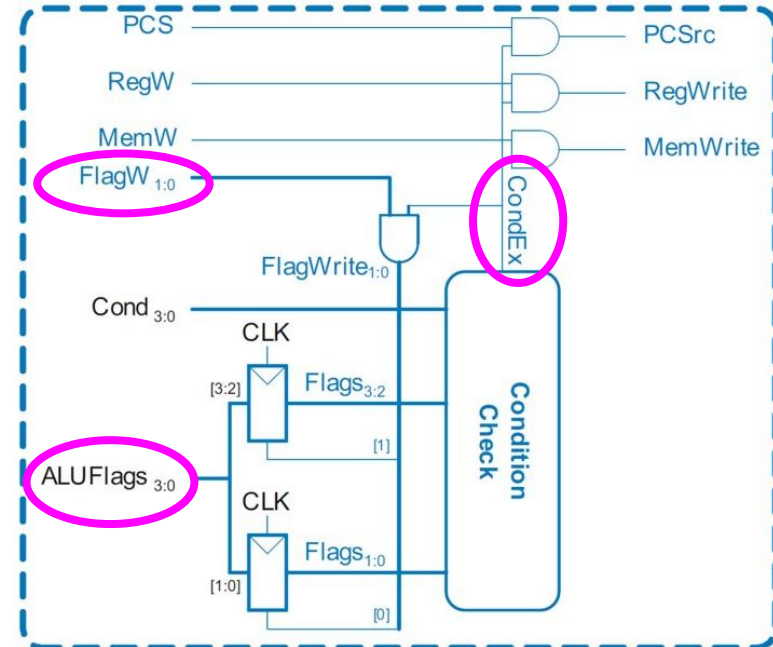- Only Flags_{3:2} updated
- i.e., only NZ Flags updated




Example: ORR

Op	Funct _s	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1

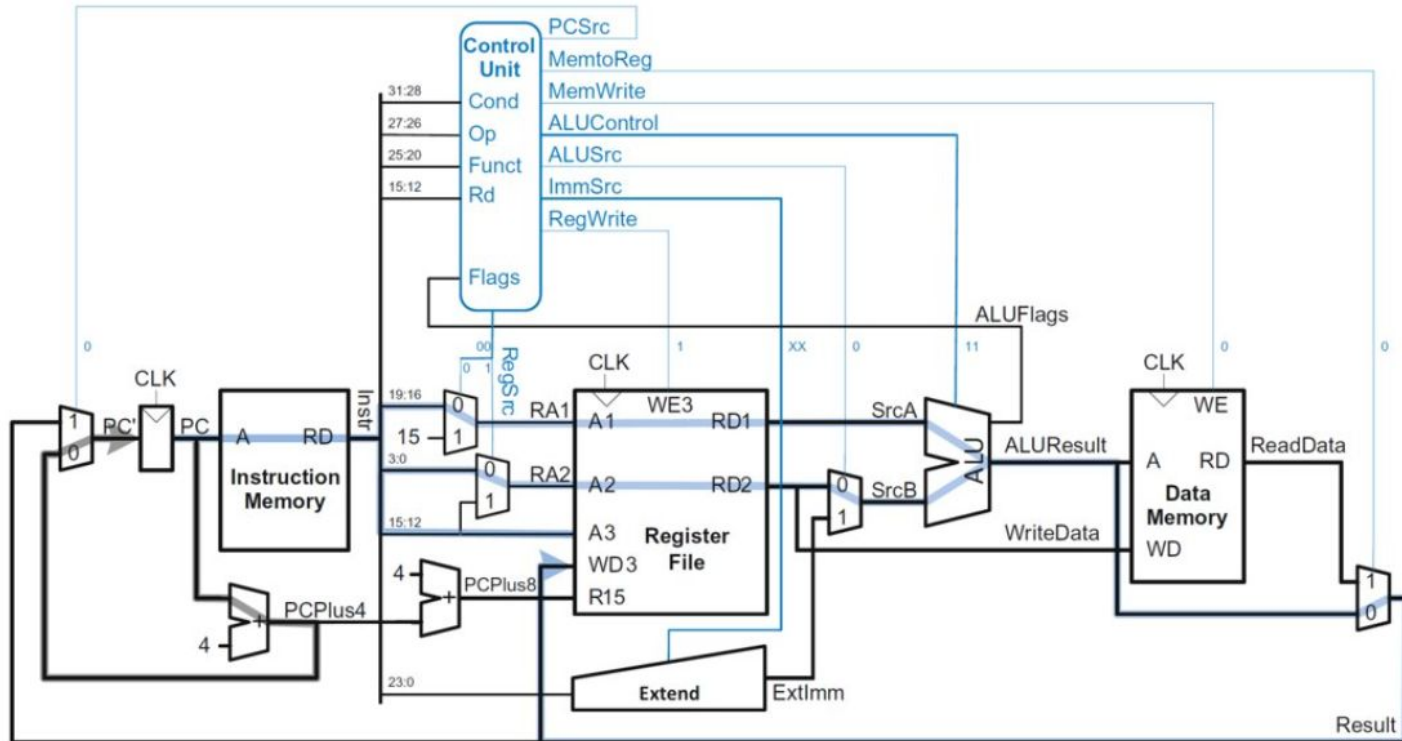


Extended Functionality: CMP

No change to datapath

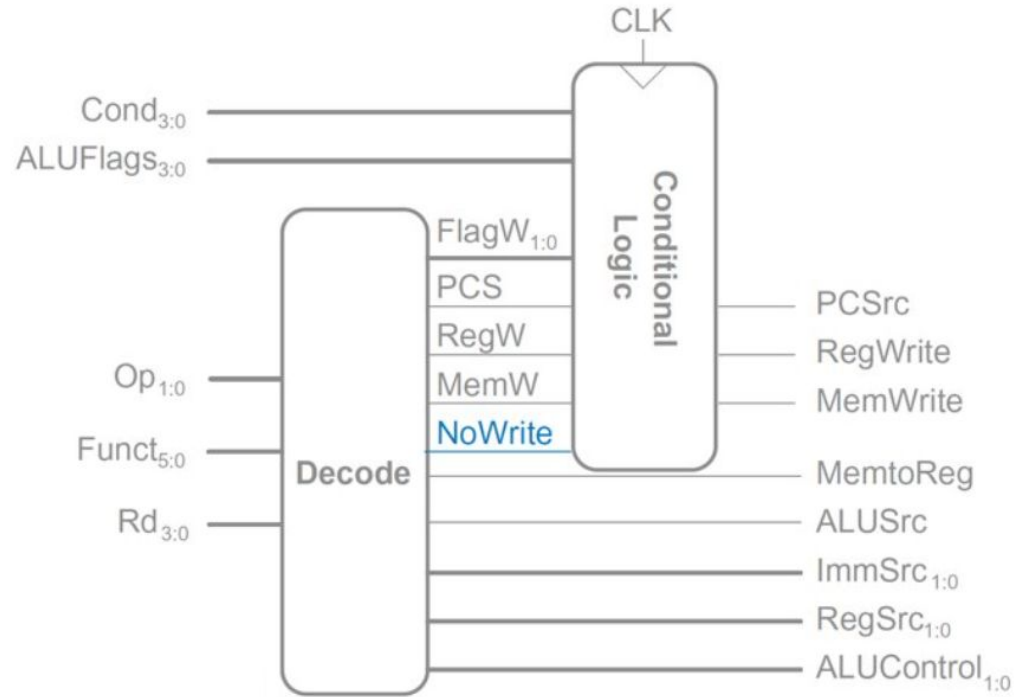

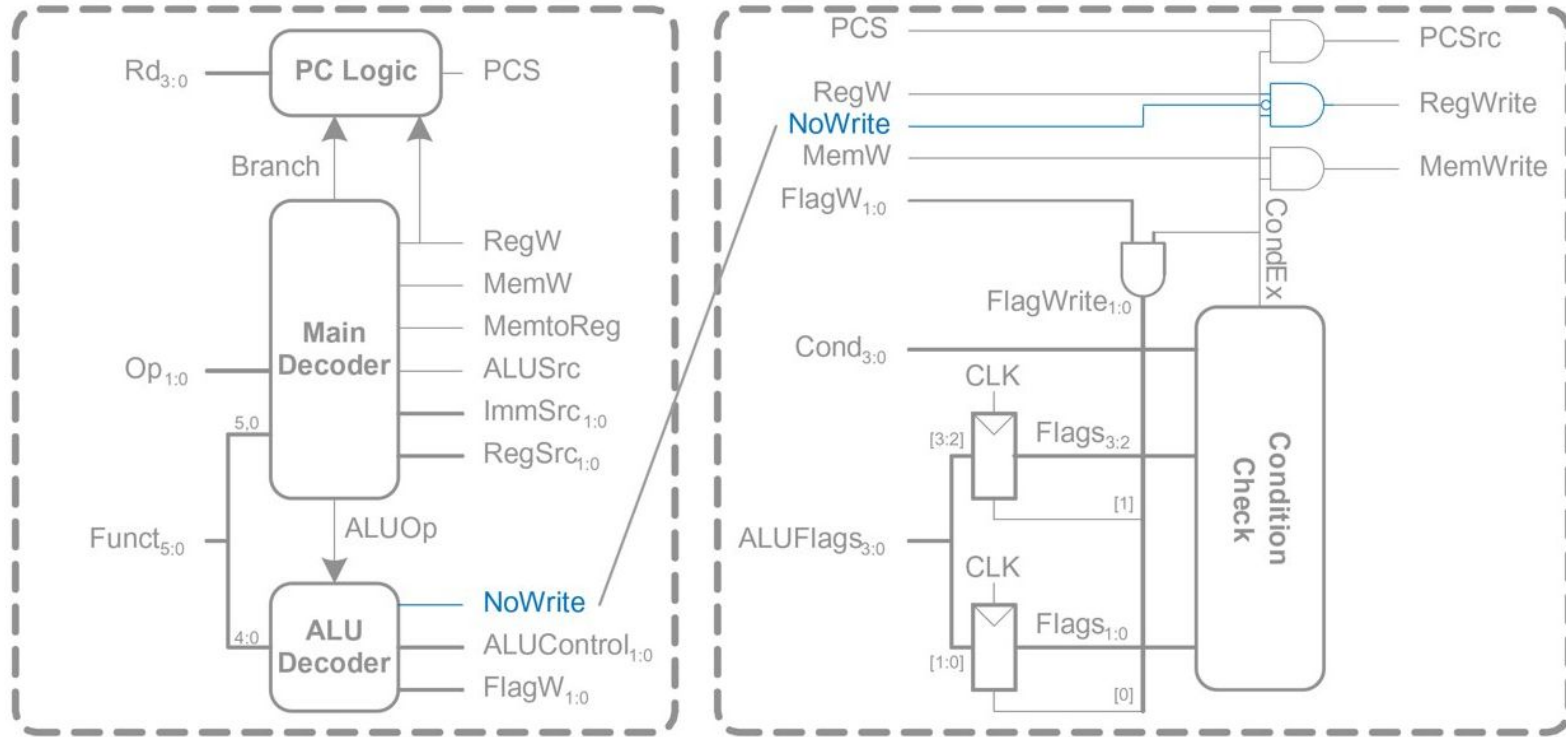Extended Functionality: CMP (look inside)




Extended Functionality: CMP

ALUOp	Func _{4:1} (cmd)	Func ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}	NoWrite
0	X	X	Not DP	00	00	0
1	0100	0	ADD	00	00	0
		1			11	0
	0010	0	SUB	01	00	0
		1			11	0
	0000	0	AND	10	00	0
		1			10	0
	1100	0	ORR	11	00	0
		1			10	0
	1010	1	CMP	01	11	1


Extended Functionality: Shifted Register

No change to controller

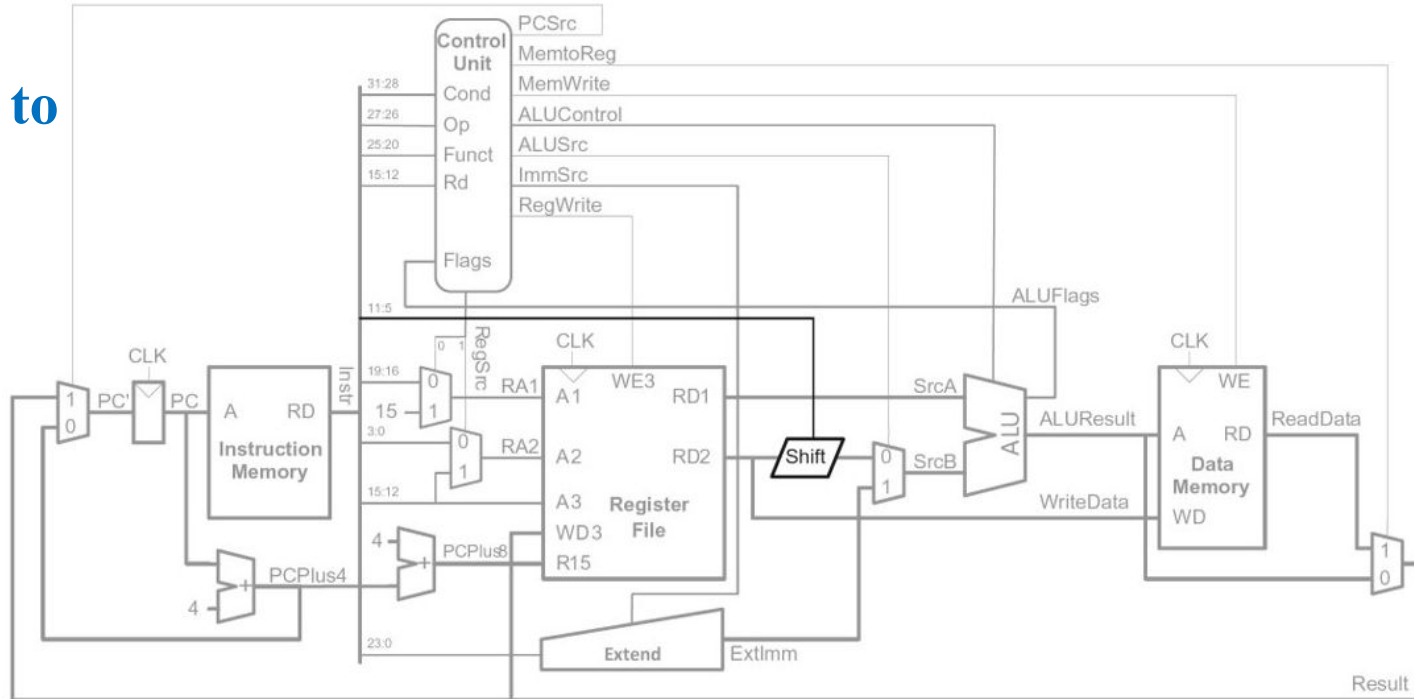

ADD R7, R2, R12, LSR #5

31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0
14	0	0	4	0	2	7	5	01	2	0 12
cond	op	I	cmd	S	rn	rd	shamt5	sh		rm

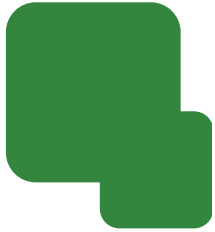

Processor Performance

Processor Performance


Program Execution Time

$$= (\# \text{instructions}) (\text{cycles/instruction}) (\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times \text{TC}$$

Single-Cycle Performance

TC limited by critical path (LDR)

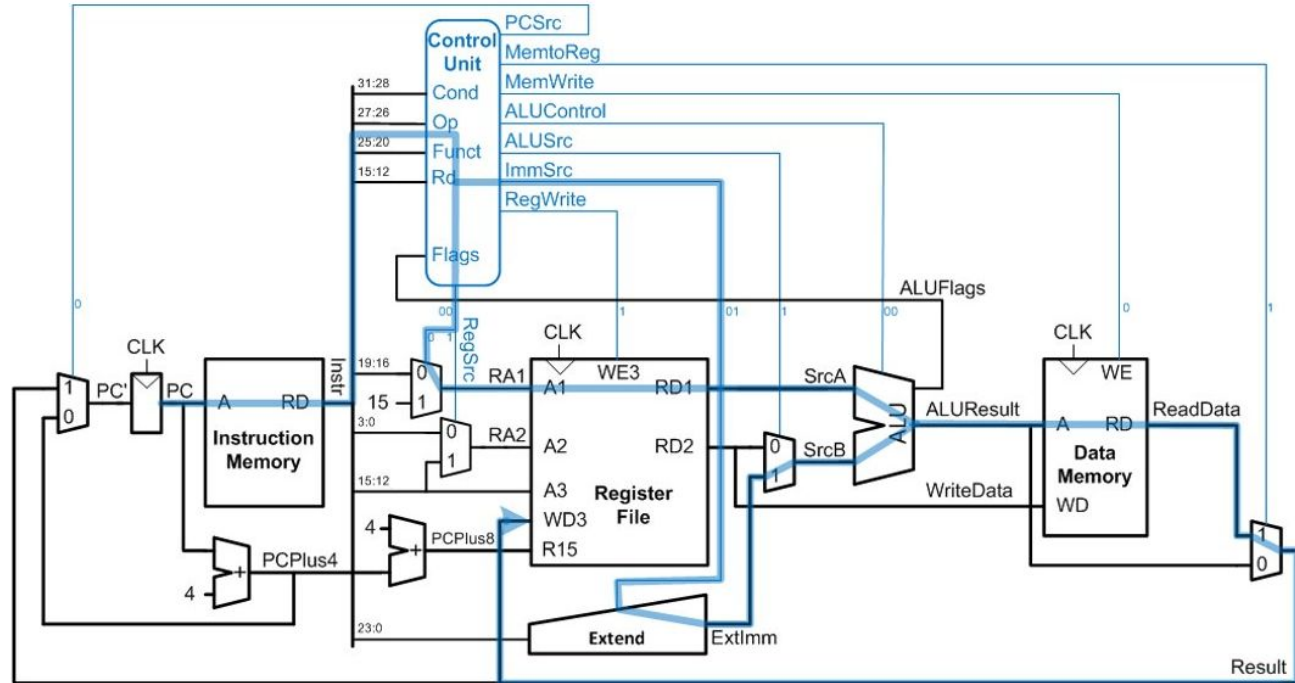

Single-Cycle Performance

- Single-cycle critical path:

$$T_{c1} = t_{pcq_PC} + t_{mem} + t_{dec} + \max[t_{mux} + t_{Rfread}, t_{setup} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- Typically, limiting paths are:

- memory, ALU, register file
- $T_{c1} = t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{Rfread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{Rfread}	100
Register file setup	$t_{RFsetup}$	60

Single-Cycle Performance Example

$$T_{c1} = ?$$

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

Single-Cycle Performance Example

$$\begin{aligned}T_{c1} &= t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\&= [50 + 2(200) + 70 + 100 + 120 + 2(25) + 60] \text{ ps} \\&= 840 \text{ ps}\end{aligned}$$

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1)(840 \times 10^{-12} \text{ s}) \\ &= 84 \text{ seconds}\end{aligned}$$

Multicycle ARM Processor